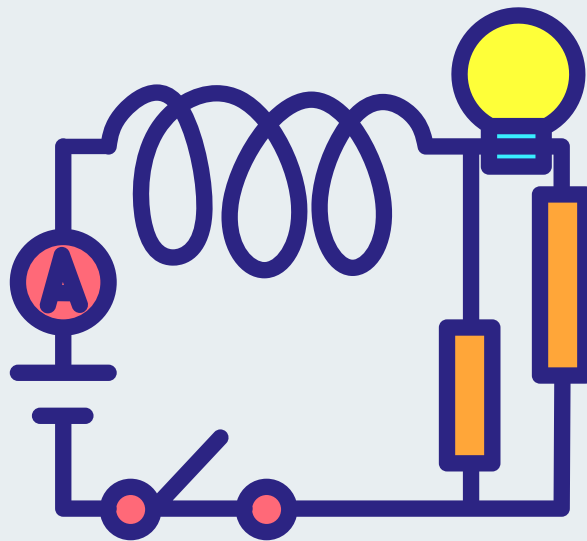


# PHYSICS

ENTHUSIAST | LEADER | ACHIEVER



## EXERCISE

### Current Electricity

---

ENGLISH MEDIUM

---

**EXERCISE-I (Conceptual Questions)****Build Up Your Understanding****ELECTRIC CURRENT & DRIFT VELOCITY**

1. If  $10^6$  electrons/s are flowing through an area of cross section of  $10^{-4} \text{ m}^2$  then the current will be :-  
 (1)  $1.6 \times 10^{-7} \text{ A}$  (2)  $1.6 \times 10^{-13} \text{ A}$   
 (3)  $1 \times 10^{-6} \text{ A}$  (4)  $1 \times 10^2 \text{ A}$

**CE0001**

2. The current in a conductor varies with time  $t$  as  $I = 2t + 3t^2 \text{ A}$  where  $I$  is amperes and  $t$  in seconds. Electric charge flowing through a section of the conductor during  $t = 2 \text{ s}$  to  $t = 3 \text{ s}$  is :-  
 (1) 10 C (2) 24 C  
 (3) 33 C (4) 44 C

**CE0002**

3. 10,000 electrons are passing per minute through a tube of radius 1cm. The resulting current is :  
 (1) 10000 A (2)  $0.25 \times 10^{-16} \text{ A}$   
 (3)  $10^{-9} \text{ A}$  (4)  $0.5 \times 10^{-19} \text{ A}$

**CE0003**

4. There are  $8.4 \times 10^{22}$  free electrons per  $\text{cm}^3$  in copper. The current in the wire is 0.21 A ( $e = 1.6 \times 10^{-19} \text{ C}$ ). Then the drifts velocity of electrons in a copper wire of  $1 \text{ mm}^2$  cross section, will be :-  
 (1)  $2.12 \times 10^{-5} \text{ m/s}$   
 (2)  $0.78 \times 10^{-5} \text{ m/s}$   
 (3)  $1.56 \times 10^{-5} \text{ m/s}$   
 (4) none of these

**CE0004**

5. There is a current of 40 amperes in a wire of  $10^{-6} \text{ m}^2$  area of cross-section. If the number of free electrons per  $\text{m}^3$  is  $10^{29}$ , then the drift velocity will be  
 (1)  $1.25 \times 10^3 \text{ m/s}$  (2)  $2.50 \times 10^{-3} \text{ m/s}$   
 (3)  $25.0 \times 10^{-3} \text{ m/s}$  (4)  $250 \times 10^{-3} \text{ m/s}$

**CE0005**

6. S.I. unit of current is :-  
 (1) C (2) A (3) A/s (4) N/s

**CE0006**

7. When no current flows through a conductor :-  
 (1) the free electrons do not move  
 (2) the average speed of a free electron over a large period of time is zero  
 (3) the average velocity of a free electron over a large period of time is zero  
 (4) the average of square of velocities of all the free electrons at an instant is zero

**CE0007**

8. The number of free electrons per 10 mm of an ordinary copper wire is about  $2 \times 10^{21}$ . The average drift speed of the electrons is 0.25 mm/s The current flowing is :-  
 (1) 0.8 A (2) 8 A (3) 80 A (4) 5 A

**CE0009**

9. In a Neon discharge tube  $2.9 \times 10^{18} \text{ Ne}^+$  ions move to the right each second, while  $1.2 \times 10^{18}$  electrons move to the left per second; electron charge is  $1.6 \times 10^{-19} \text{ C}$ . The current in the discharge tube is :-  
 (1) 1 A towards right  
 (2) 0.66 A towards right  
 (3) 0.66 A towards left  
 (4) zero

**CE0010**


10. Two wires each of radius of cross section  $r$  but of different materials are connected together end to end (in series). If the densities of charge carriers in the two wires are in the ratio 1:4, the drift velocity of electrons in the two wires will be in the ratio :  
 (1) 1 : 2 (2) 2 : 1  
 (3) 4 : 1 (4) 1 : 4

**CE0011**

11. A current  $I$  flows through a uniform wire of diameter  $d$  when the electron drift velocity is  $v$ . The same current will flow through a wire of diameter  $d/2$  made of the same material if the drift velocity of the electrons is  
 (1)  $v/4$  (2)  $v/2$  (3)  $2v$  (4)  $4v$

**CE0012**

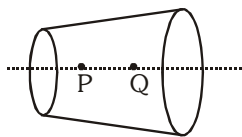
12. A wire has a non-uniform cross-section as shown in figure. A steady current flows through it. The drift speed of electrons at points P and Q is  $v_P$  and  $v_Q$ , then :-



- (1)  $v_P = v_Q$  (2)  $v_P < v_Q$   
(3)  $v_P > v_Q$  (4) data is insufficient

CE0013

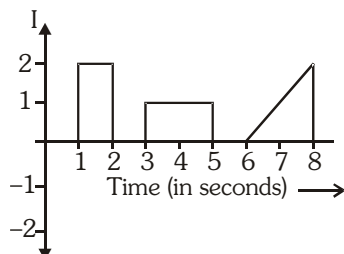13. The plot represents the flow of current through a wire for different time intervals. The ratio of charges flowing through the wire corresponding to these time intervals is (see figure) :-



- (1) 2 : 1 : 2 (2) 1 : 3 : 3  
(3) 1 : 1 : 1 (4) 2 : 3 : 4

CE0014

### OHM'S LAW & ELECTRICAL RESISTANCE

14. Three copper wires are there with lengths and cross-sectional areas as  $(\ell, A)$ ;  $(2\ell, \frac{A}{2})$  and  $(\frac{\ell}{2}, 2A)$ . Resistance :-

- (1) minimum for the wire of cross-sectional area  $\frac{A}{2}$   
(2) minimum for the wire of cross-sectional area A  
(3) minimum for the wire of cross-sectional area 2A  
(4) same for all the three cases.

CE0015

15. A wire of uniform cross-section A, length  $\ell$  and resistance R is bent into a complete circle; the resistance between any two of diametrically opposite points will be :-

- (1)  $\frac{R}{2}$  (2)  $\frac{R}{4}$  (3)  $\frac{R}{8}$  (4) 4R

CE0016

16. The electric resistance of a certain wire of iron is R. If its length and radius both are doubled, then :-

- (1) the resistance will be halved and the specific resistance will remain unchanged  
(2) the resistance will be halved and the specific resistance will be doubled  
(3) the resistance and the specific resistance, will both remain unchanged  
(4) the resistance will be doubled and the specific resistance will be halved.

CE0017

17. When a piece of aluminium wire of finite length is drawn to reduce its diameter to half its original value, its resistance will become :-

- (1) two times  
(2) four times  
(3) eight times  
(4) sixteen times

CE0018

18. As the temperature of a metallic resistor is increased, the product of resistivity and conductivity :-

- (1) increases  
(2) decreases  
(3) may increase or decrease  
(4) remains constant.

CE0019

19. If a wire is stretched, so that its length is 20% more than its initial length, the percentage increase in the resistance of the wire is :-

- (1) 40% (2) 10%  
(3) 44% (4) 25%

CE0020

20. The length of a given cylindrical wire is increased by 100%. Due to the consequent decrease in diameter the change in the resistance of the wire will be :-


- (1) 300% (2) 200%  
(3) 100% (4) 50%

CE0021

21. On increasing the temperature, the specific resistance of a conductor and a semiconductor-
- (1) both increase
  - (2) both decrease
  - (3) increases and decreases respectively
  - (4) decreases and increases respectively

CE0022

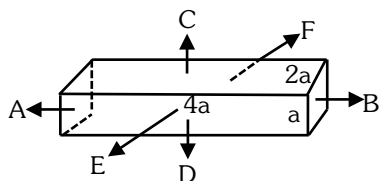22. A conductor with rectangular cross section has dimensions ( $a \times 2a \times 4a$ ) as shown in figure. Resistance across AB is  $x$ , across CD is  $y$  and across EF is  $z$ . Then



- (1)  $x = y = z$
- (2)  $x > y > z$
- (3)  $y > x > z$
- (4)  $x > z > y$

CE0023

23. Specific resistance of a conductor increases with:-
- (1) increase in temperature.
  - (2) increase in cross-sectional area
  - (3) increase in cross-sectional area and decrease in length.
  - (4) decrease in cross-sectional area.


CE0024

24. The temperature coefficient of resistance of a wire is 0.00125 per degree celcius. At 300 K its resistance is 1 ohm. The resistance of the wire will be 2 ohms at a temperature :-
- (1) 1154 K
  - (2) 1127 K
  - (3) 600 K
  - (4) 1400 K

CE0025

25. The current voltage graph for a given metallic conductor at two different temperatures  $T_1$  and  $T_2$  are as shown in the figure. Then :-

- (1)  $T_1 > T_2$
- (2)  $T_1 = T_2$
- (3) nothing can be said about  $T_1$  and  $T_2$
- (4)  $T_1 < T_2$

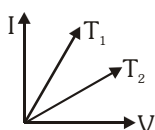

CE0026

26. The effective resistance is  $\frac{6}{5} \Omega$ , when two wires are joined in parallel. When one of the wire breaks, the effective resistance is 2 ohms. The resistance of the broken wire was :-
- (1)  $\frac{3}{5} \Omega$
  - (2)  $2 \Omega$
  - (3)  $\frac{6}{5} \Omega$
  - (4)  $3 \Omega$

CE0027

27. At what temperature will the resistance of a copper wire become three times its value at  $0^\circ \text{C}$ ? [Temperature coefficient of resistance for copper =  $4 \times 10^{-3}$  per  $^\circ \text{C}$ ] :-
- (1)  $400^\circ \text{C}$
  - (2)  $450^\circ \text{C}$
  - (3)  $500^\circ \text{C}$
  - (4)  $600^\circ \text{C}$

CE0028

28. Copper and silicon are cooled from 300 K to 60 K; the specific resistance :-
- (1) decreases in copper but increases in silicon
  - (2) increases in copper but decreases in silicon
  - (3) increases in both
  - (4) decreases in both

CE0029

29. Two resistances  $R_1$  and  $R_2$  are made of different materials. The temperature coefficient of the material of  $R_1$  is  $\alpha$  and that of the material of  $R_2$  is  $-\beta$ . The resistance of the series combination of  $R_1$  and  $R_2$  does not change with temperature, then the ratio of resistances of the two wires at  $0^\circ \text{C}$  will be :

- (1)  $\frac{\alpha}{\beta}$
- (2)  $\frac{\alpha + \beta}{\alpha - \beta}$
- (3)  $\frac{\alpha^2 + \beta^2}{\alpha\beta}$
- (4)  $\frac{\beta}{\alpha}$

CE0030

### COMBINATION OF RESISTANCES & KIRCHHOFF'S LAW

30. A metal wire of resistance  $R$  is cut into three equal pieces which are then connected side by side to form a new wire, the length of which is equal to one third of the original length. The resistance of this new wire is :-

- (1)  $R$
- (2)  $3R$
- (3)  $\frac{R}{9}$
- (4)  $\frac{R}{3}$

CE0031


- 31.** Three resistances of values  $2\ \Omega$ ,  $3\ \Omega$  and  $6\ \Omega$  are to be connected to yield an effective resistance of  $4\ \Omega$ . This can be done by connecting :

- (1)  $3\ \Omega$  resistance in series with a parallel combination of  $2\ \Omega$  and  $6\ \Omega$
- (2)  $6\ \Omega$  resistance in series with a parallel combination of  $2\ \Omega$  and  $3\ \Omega$
- (3)  $2\ \Omega$  resistance in series with a parallel combination of  $3\ \Omega$  and  $6\ \Omega$
- (4)  $2\ \Omega$  resistance in parallel with a parallel combination of  $3\ \Omega$  and  $6\ \Omega$

**CE0032**

- 32.** What will be the equivalent resistance between the points A and D ?


- (1)  $10\ \Omega$
- (2)  $20\ \Omega$
- (3)  $30\ \Omega$
- (4)  $40\ \Omega$

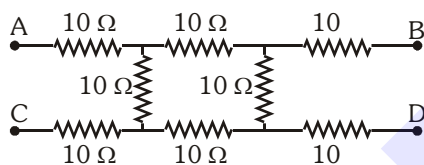

**CE0033**

- 33.** In the circuit shown here, what is the value of the unknown resistance  $R$  so that the total resistance of the circuit between points 'P' and 'Q' is also equal to  $R$  :-


- (1)  $3\ \Omega$
- (2)  $\sqrt{39}\ \Omega$
- (3)  $\sqrt{69}\ \Omega$
- (4)  $10\ \Omega$

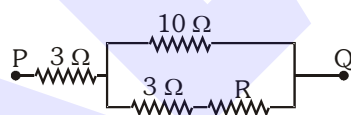

**CE0034**


- 34.** The resistance across P and Q in the given figure is

- (1)  $\frac{R}{3}$
- (2)  $\frac{R}{2}$
- (3)  $2R$
- (4)  $6R$

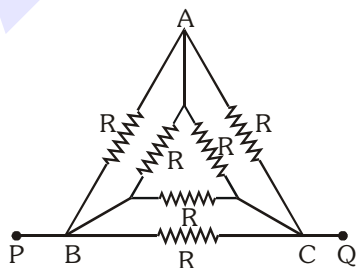

**CE0035**

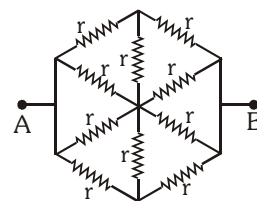- 35.** The resistance of the circuit between A and B is :




- (1)  $r$
- (2)  $0.5r$
- (3)  $2r$
- (4)  $3r$

**CE0036**

- 36.** Thirteen resistances each of resistance  $R\ \Omega$  are connected in the circuit as shown in the figure. The effective resistance between A and B is :-


- (1)  $\frac{4R}{3}\ \Omega$
- (2)  $2R\ \Omega$
- (3)  $R\ \Omega$
- (4)  $\frac{2R}{3}\ \Omega$

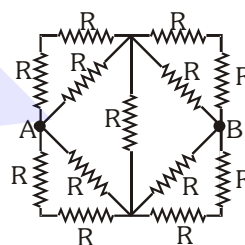

**CE0037**

- 37.** The total resistance between x and y in ohms is:-

- (1)  $1\ \Omega$
- (2)  $4\ \Omega$
- (3)  $\frac{4}{3}\ \Omega$
- (4)  $\frac{2}{3}\ \Omega$

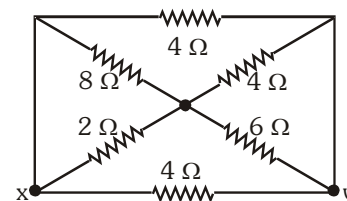


**CE0038**

- 38.** The resultant resistance of  $n$  wires each of resistance  $r$  ohms is  $R$ , when they are connected in parallel. When these  $n$  resistances are connected in series, the resultant resistance will be :-

- (1)  $\frac{R}{n}$
- (2)  $\frac{R}{n^2}$
- (3)  $nR$
- (4)  $n^2R$

**CE0039**

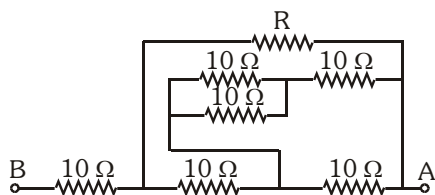
39. For the network of resistance shown in the fig. the equivalent resistance of the network between the points A and B is  $18\ \Omega$ . The value of unknown resistance R is :-



- (1)  $8\ \Omega$  (2)  $10\ \Omega$  (3)  $16\ \Omega$  (4)  $24\ \Omega$

CE0040

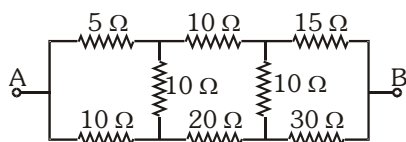
40. In the arrangement of resistances shown below, the effective resistance between points A and B is



- (1)  $20\ \Omega$  (2)  $30\ \Omega$  (3)  $90\ \Omega$  (4)  $110\ \Omega$

CE0041

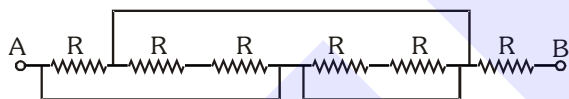
41. In the circuit shown the equivalent resistance between A and B is



- (1) R (2)  $2R/5$  (3)  $R/3$  (4)  $2R$

CE0042

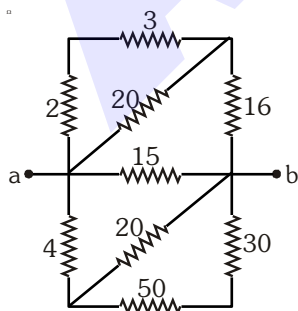
42. In the figure the numerical values denote resistances in SI units. The total resistance of the circuit between a & b will be:



- (1) 12 ohms (2) 24 ohms.  
(3) 15 ohms (4) 6 ohms

CE0043

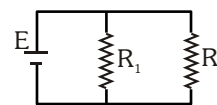
43. Resistors  $R_1$  and  $R_2$  have an equivalent resistance of 6 ohms when connected in the circuit shown below. The resistance of  $R_1$  could be (in  $\Omega$ ) :-



- (1) 1 (2) 5 (3) 8 (4) 4

CE0044

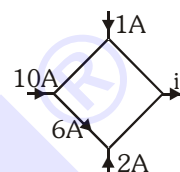
44. Value of current i in the following circuit is :-



- (1) 13 A (2) 12 A  
(3) 9 A (4) none of the above

CE0045

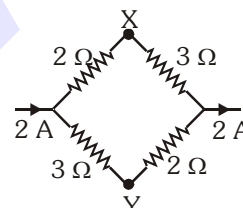
45. The potential difference between X and Y in volts is :-



- (1) 1 (2) -1 (3) 2 (4) -2

CE0046

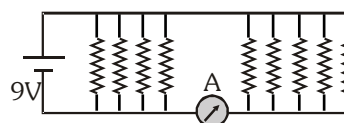
46. If each resistance in the fig. is of  $9\ \Omega$  then reading of the ammeter is :-



- (1) 5 A (2) 8 A (3) 2 A (4) 9 A

CE0047

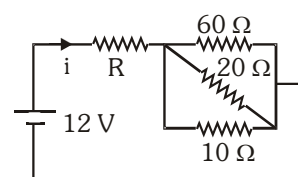
47. If  $i = 0.25\text{ A}$  in figure, then value of R is :-



- (1)  $48\ \Omega$  (2)  $12\ \Omega$  (3)  $120\ \Omega$  (4)  $42\ \Omega$

CE0048

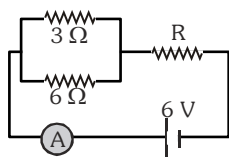
48. If the ammeter in the given circuit reads 2 A, the resistance R is :-



- (1) 1 ohms (2) 2 ohms  
(3) 3 ohms (4) 4 ohms

**CE0049**

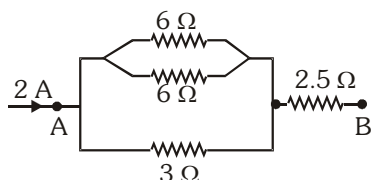
49. The equivalent resistance and potential difference between A and B for the circuit are respectively :-



- (1) 4 Ω, 8 V (2) 8 Ω, 4 V  
(3) 2 Ω, 2 V (4) 16 Ω, 8 V

**CE0050**

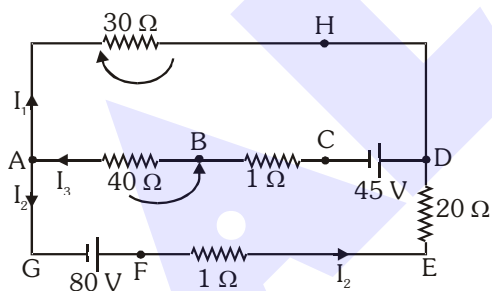
50. For the current loops shown in the figure, Kirchhoff's loop rule for the loops AHDCBA and AHDEFGA yields these equations respectively :-



- (1)  $-30 I_1 - 41 I_3 + 45 = 0$  and  $-30 I_1 + 21 I_2 - 80 = 0$   
(2)  $30 I_1 - 41 I_3 + 45 = 0$  and  $30 I_1 - 21 I_2 - 80 = 0$   
(3)  $30 I_1 + 41 I_3 - 45 = 0$  and  $-30 I_1 + 21 I_2 + 80 = 0$   
(4)  $-30 I_1 - 41 I_3 - 45 = 0$  and  $-30 I_1 + 21 I_2 - 80 = 0$

**CE0051**

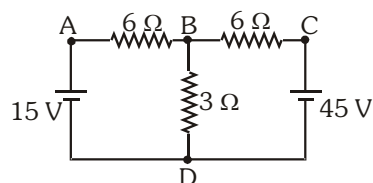
51. In the circuit shown in figure, find the current through the branch BD.



- (1) 1 A (2) 5 A  
(3) 3 A (4) 7 A

**CE0052**

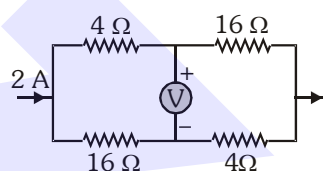52. In the circuit shown below, the reading of the voltmeter V is :-




- (1) 12 V (2) 8 V (3) 20 V (4) 16 V

**CE0053**


53. Find the potential of J with respect of G :-

- (1) 40 V  
(2) 60 V  
(3) 20 V  
(4) 30 V

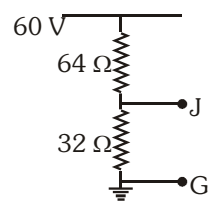

**CE0054**

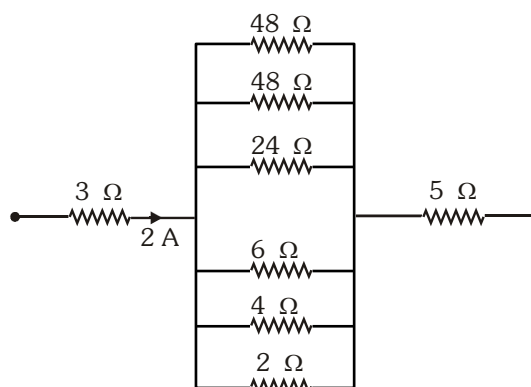54. Find the potential difference across the 24 Ω :-




- (1) 48 volts (2) 2 volts  
(3) 4 volts (4) 1 volts

**CE0055**




55. In a network as shown in the figure the potential difference across the resistance  $2R$  is (the cell has an emf  $E$  with no internal resistance) :

- (1)  $2E$   
 (2)  $\frac{4E}{7}$   
 (3)  $\frac{E}{7}$   
 (4)  $E$

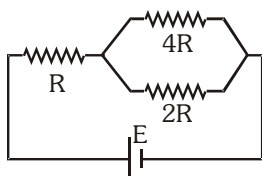

CE0056

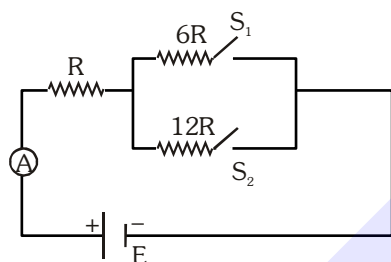
56. The reading of ammeter is  $I_1$  when only  $S_1$  is closed and  $I_2$  when only  $S_2$  is closed. The reading is  $I_3$  when both  $S_1$  &  $S_2$  are closed simultaneously then :-



- (1)  $I_1 > I_2 > I_3$       (2)  $I_2 > I_3 > I_1$   
 (3)  $I_3 > I_2 > I_1$       (4)  $I_3 > I_1 > I_2$

CE0057

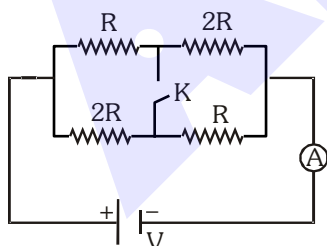
57. How will the reading of ammeter change if the key  $k$  is closed ?



- (1) Increase  
 (2) Decrease  
 (3) Remains same  
 (4) Information insufficient

CE0058

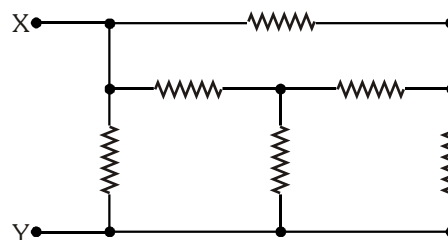58. Six resistors each of  $10\ \Omega$  are connected as shown. The equivalent resistance between points X and Y is :




- (1)  $20\ \Omega$       (2)  $5\ \Omega$       (3)  $25/3\ \Omega$       (4)  $10\ \Omega$

CE0059


59. Five equal resistances each of resistance  $R$  are connected as shown in the Figure. A battery of voltage  $V$  is connected between A and B. The current flowing in AFCEB will be

- (1)  $\frac{V}{R}$   
 (2)  $\frac{V}{2R}$   
 (3)  $\frac{2V}{R}$   
 (4)  $\frac{3V}{R}$

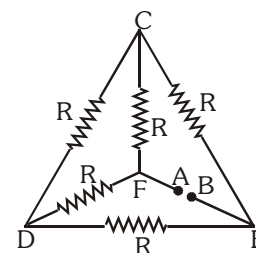

CE0060

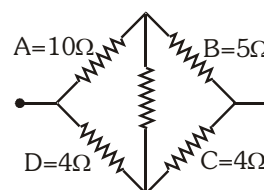60. In a typical Wheatstone bridge the resistance in cyclic order are  $A = 10\ \Omega$ ,  $B = 5\ \Omega$ ,  $C = 4\ \Omega$  and  $D = 4\ \Omega$ . For the bridge to be balanced :




- (a)  $10\ \Omega$  should be connected in parallel with A  
 (b)  $10\ \Omega$  should be connected in series with A  
 (c)  $5\ \Omega$  should be connected in series with B  
 (d)  $5\ \Omega$  should be connected in parallel with B  
 (1) a, b      (2) b, c      (3) a, c      (4) all

CE0061



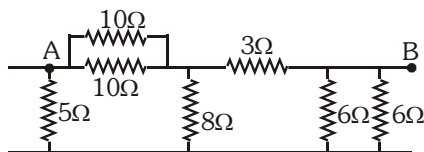
61. Seven resistances are connected as shown in the figure. The equivalent resistance between A and B is :-



- (1)  $3\ \Omega$       (2)  $4\ \Omega$       (3)  $4.5\ \Omega$       (4)  $5\ \Omega$

**CE0062**

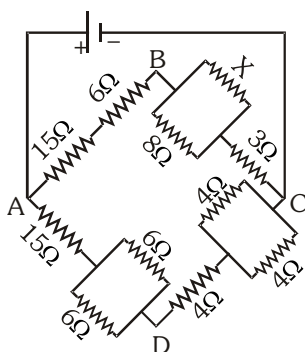
62. In the following circuit diagram the value of resistance X for the potential difference between B and D to be zero is :-



- (1) 4 ohms      (2) 6 ohms  
(3) 8 ohms      (4) 9 ohms

**CE0063**

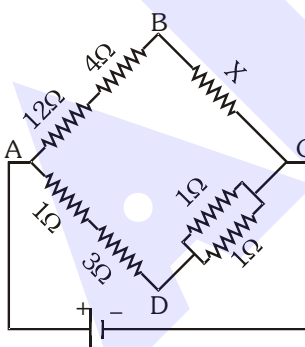63. In the arrangement of resistances shown in the circuit, the potential difference between points B and D will be zero, when the unknown resistance X is :-



- (1)  $4\ \Omega$       (2)  $3\ \Omega$       (3)  $2\ \Omega$       (4)  $1\ \Omega$

**CE0064**


64. The resistance of each arm of a Wheat stone bridge is  $10\ \Omega$ . A resistance of  $10\ \Omega$  is connected in series with the galvanometer then the equivalent resistance across the battery will be :-

- (1)  $10\ \Omega$       (2)  $15\ \Omega$       (3)  $20\ \Omega$       (4)  $40\ \Omega$

**CE0065**

65. For the network shown in the figure the value of the current i is :-

- (1)  $\frac{18V}{5}$   
(2)  $\frac{5V}{9}$   
(3)  $\frac{9V}{35}$   
(4)  $\frac{5V}{18}$

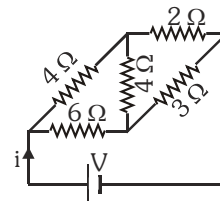


**CE0066**

### CELLS & COMBINATION OF CELLS, ELECTRIC POWER & ENERGY

66. Two cells X and Y are connected to a resistance of  $10\ \Omega$  as shown in the figure. The terminal voltage of cell Y is :-

- (1) zero  
(2) 2 V  
(3) 4 V  
(4) 10 V

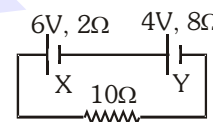

**CE0067**

67. A battery has e.m.f. 4 V and internal resistance 'r'. When this battery is connected to an external resistance of 2 ohms, a current of 1 A flows in the circuit. What current will flow if the terminals of the battery are connected directly ?

- (1) 1 A      (2) 2 A  
(3) 4 A      (4) infinite

**CE0068**

68. Internal resistance of primary cell depends on :-

- (1) the nature of electrolyte  
(2) the area of plates immersed in the electrolyte  
(3) the concentration of electrolyte and distance between the plates  
(4) all the above

**CE0069**

69. The potential difference between the terminals of a cell is found to be 3 volts when it is connected to a resistance of value equal to its internal resistance. The e.m.f. of the cell is :-

- (1) 3 V      (2) 6 V      (3) 1.5 V      (4) 4.5 V

**CE0070**


70. A current of 2 A is flowing through a cell of e.m.f. 5 V and internal resistance  $0.5 \Omega$  from negative to positive electrode. If the potential of negative electrode is 10 V, the potential of positive electrode will be :-

(1) 5 V (2) 14 V (3) 15 V (4) 16 V

CE0071

71. In the following circuit if  $V_A - V_B = 4$  V, then the value of resistance X in ohms will be :-

(1) 5  
(2) 10  
(3) 15  
(4) 20

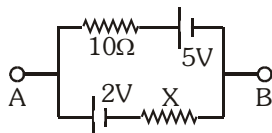

CE0072

72. Electromotive force of a cell is basically a

(1) force (2) power  
(3) work (4) current capacity

CE0073

73. The terminal voltage is  $\frac{E}{2}$  when a current of 2 A is flowing through  $2 \Omega$  resistance; the internal resistance of the cell is :-

(1)  $1 \Omega$  (2)  $2 \Omega$  (3)  $3 \Omega$  (4)  $4 \Omega$


CE0074

74. When a resistance of 2 ohms is connected across the terminals of a cell, the current is 0.5 A. When the resistance is increased to 5 ohms, the current becomes 0.25 A. The e.m.f. of the cell is:-

(1) 1.0 V (2) 1.5 V (3) 2.0 V (4) 2.5 V

CE0075

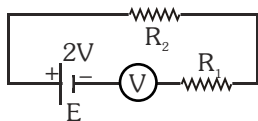75. A cell of e.m.f. 2 V and negligible internal resistance is connected to resistors  $R_1$  and  $R_2$  as shown in the figure. The resistance of the voltmeter,  $R_1$  and  $R_2$  are  $80 \Omega$ ,  $40 \Omega$  and  $80 \Omega$  respectively. The reading of the voltmeter is :



(1) 1.78 V (2) 1.60 V  
(3) 0.80 V (4) 1.33 V

CE0076

76. A cell supplies a current of 0.9 A through a  $2 \Omega$  resistor and a current of 0.3 A through a  $7 \Omega$  resistor. The internal resistance of the cell is :-

(1)  $1.0 \Omega$  (2)  $0.5 \Omega$   
(3)  $2.0 \Omega$  (4)  $1.2 \Omega$

CE0077

77. A 10 V battery with internal resistance  $0.5 \Omega$  is connected across a variable resistance R. The value of R for which the power delivered to it is maximum, is equal to :-

(1)  $0.5 \Omega$  (2)  $1 \Omega$  (3)  $1.5 \Omega$  (4)  $2 \Omega$





CE0078

78. An electric bulb is designed to draw a power  $P_0$  at voltage  $V_0$ . If the voltage is V, it draws a power P, then -

(1)  $P = \left(\frac{V}{V_0}\right) P_0$  (2)  $P = \left(\frac{V_0}{V}\right) P_0$   
(3)  $P = \left(\frac{V_0}{V}\right)^2 P_0$  (4)  $P = \left(\frac{V}{V_0}\right)^2 P_0$


CE0079

79. Consider the four circuits shown in the figure below. In which circuit power dissipated maximum (Neglect the internal resistance of the power supply)

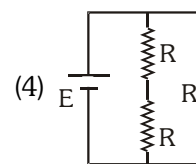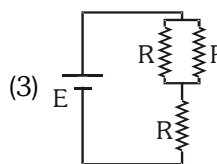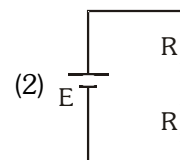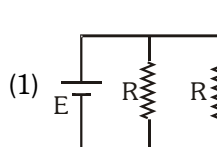

CE0080

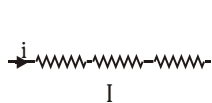- 80.** Three resistances of equal value are arranged in different combinations as shown below. Arrange them in the increasing order of power dissipation:




I



II



III

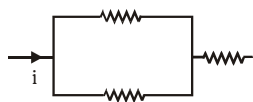

IV

- (1)  $\text{III} < \text{II} < \text{IV} < \text{I}$  (2)  $\text{II} < \text{III} < \text{IV} < \text{I}$   
(3)  $\text{I} < \text{IV} < \text{III} < \text{II}$  (4)  $\text{I} < \text{III} < \text{II} < \text{IV}$

**CE0081**

- 81.** 25 W, 200 V and 100 W, 200 V bulbs are connected in series to a source of 400 volts. Which bulb will fuse ?
- (1) 25 W  
(2) 100 W  
(3) Both will fuse at the same time  
(4) None of the bulbs will fuse

**CE0082**


- 82.** You are provided with 48 cells, each of emf 2 volts and internal resistance 4 ohms. What maximum current can flow in the circuit having an external resistance of  $12 \Omega$  ?
- (1) 1 A (2) 1.2 A  
(3) 0.96 A (4) 1.08 A

**CE0083**


- 83.** two electric bulbs of the same power, but with different marked voltages are connected in series across a power line. Their brightness will be :-
- (1) directly proportional to their marked voltages  
(2) inversely proportional to their marked voltages  
(3) directly proportional to the squares of their marked voltages  
(4) inversely proportional to the squares of their marked voltages

**CE0084**

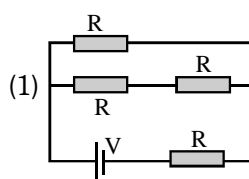
- 84.** Four circuits are shown below. All the batteries have the same voltage  $V$  and all resistors have the same resistance  $R$ . In which circuit does the battery delivers the most power?




(1)

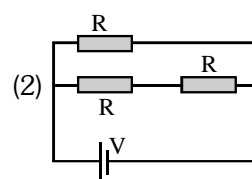

(2)

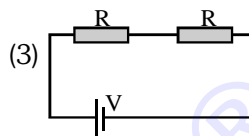

(3)

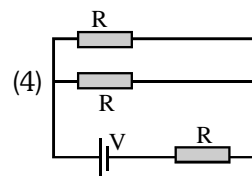


(4)

**CE0085**

- 85.** Two cells, each of e.m.f.  $E$  and internal resistance  $r$ , are connected in parallel across a resistor  $R$ . The power dissipated in the resistor is maximum if :
- (1)  $R = r$  (2)  $R = 2r$   
(3)  $R = \frac{3r}{2}$  (4)  $R = \frac{r}{2}$

**CE0087**

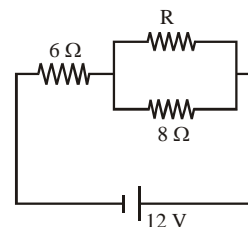
- 86.** In the circuit shown in figure, the power which is dissipated as heat in the  $6 \Omega$  resistor is 6 W. What is the value of resistance  $R$  in the circuit ?



- (1)  $6 \Omega$  (2)  $10 \Omega$  (3)  $13 \Omega$  (4)  $24 \Omega$

**CE0088**

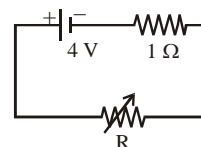- 87.** For different values of resistance,  $R$  power consumptions in  $R$  are given. Then which of the following values are not possible ?



- (a) 2 W (b) 5 W (c) 8 W (d) 4 W  
(1) Only c (2) b & c (3) a, b, c (4) All

**CE0090**

## MEASURING DEVICES

**88.** An ammeter and a voltmeter are joined in series to a cell. Their readings are A and V respectively. If a resistance is now joined in parallel with the voltmeter

- (1) both A and V will decrease
- (2) both A and V will increase
- (3) A will increase, V will decrease
- (4) A will decrease, V will increase

CE0091

**89.** A galvanometer of  $100\ \Omega$  resistance yields complete deflection when 10 mA current flows. What should be the value of shunt so that it can measure currents upto 100 mA ?

- (1)  $11.11\ \Omega$
- (2)  $9.9\ \Omega$
- (3)  $1.1\ \Omega$
- (4)  $4.4\ \Omega$

CE0092

**90.** In order to change the range of a galvanometer of  $G\ \Omega$  resistance from V volts to nV volts what will be the value of resistance in  $\Omega$  connected in series with it :-

- (1)  $(n-1)G$
- (2)  $\frac{G}{n}$
- (3)  $nG$
- (4)  $\frac{G}{n-1}$

CE0093

**91.** Resistance in the two gaps of a meter bridge are 10 ohms and 30 ohms respectively. If the resistances are interchanged, the balance point shifts by :-

- (1) 33.3 cm
- (2) 66.67 cm
- (3) 25 cm
- (4) 50 cm


CE0094

**92.** A galvanometer acting as a voltmeter will have :

- (1) a high resistance in series with its coil
- (2) a low resistance in parallel with its coil
- (3) a low resistance in series with its coil
- (4) a high resistance in parallel with its coil

CE0095

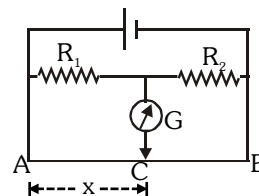**93.** In the shown arrangement of the experiment of a meter bridge if AC, corresponding to null deflection of galvanometer, is x then what would be its value if the radius of the wire AB is doubled:-




- (1) x
- (2)  $\frac{x}{4}$
- (3) 4x
- (4) 2x

CE0096

**94.** In the following circuit, the resistance of the voltmeter is  $10,000\ \Omega$  and that of the ammeter is  $20\ \Omega$ . If the reading of the ammeter is 0.1 A and that of the voltmeter is 12 V, then the value of R is :-

- (1)  $122\ \Omega$
- (2)  $100\ \Omega$
- (3)  $118\ \Omega$
- (4)  $116\ \Omega$

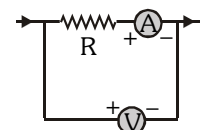

CE0097

**95.** The resistance of a galvanometer is G ohms and the range is 1 volt. The value of resistance (in  $\Omega$ ) used to convert it into a voltmeter of range 10 volts is :-

- (1) 9 G
- (2) G
- (3)  $\frac{1}{9} G$
- (4) 10 G

CE0098

**96.** A galvanometer has  $36\ \Omega$  resistance. If a 4  $\Omega$  shunt is added to this, the fraction of current that passes through the galvanometer is :-

- (1)  $\frac{1}{4}$
- (2)  $\frac{1}{9}$
- (3)  $\frac{1}{10}$
- (4)  $\frac{1}{40}$

CE0099

**97.** A galvanometer of resistance  $100\ \Omega$  gives full deflection for a current of  $10^{-5}$  A. The value of shunt required to convert it into an ammeter of range 1 ampere, is :-

- (1)  $1\ \Omega$
- (2)  $10^{-3}\ \Omega$
- (3)  $10^{-5}\ \Omega$
- (4)  $100\ \Omega$

CE0100

- 98.** There are three voltmeters of the same range but of resistances  $10000\ \Omega$ ,  $8000\ \Omega$  and  $4000\ \Omega$  respectively. The best voltmeter among these is the one whose resistance is :-

(1)  $10000\ \Omega$  (2)  $8000\ \Omega$   
(3)  $4000\ \Omega$  (4) all are equally good

**CE0101**

- 99.** 20% of the main current passes through the galvanometer. If the resistance of the galvanometer is  $G$ , then the resistance of the shunt will be :-

(1)  $\frac{G}{50}$  (2)  $\frac{G}{4}$  (3)  $50G$  (4)  $9G$

**CE0102**

- 100.** An unknown resistance  $R_1$  is connected in series with a resistance of  $10\ \Omega$ . This combination is connected to one gap of a metre bridge while a resistance  $R_2$  is connected in the other gap. The balance point is at  $50\text{ cm}$ . Now, when the  $10\ \Omega$  resistance is removed the balance point shifts to  $40\text{ cm}$ . The value of  $R_1$  is (in ohms) :-

(1) 20 (2) 10 (3) 60 (4) 40

**CE0104**

- 101.** A  $1\ \Omega$  voltmeter has a range of  $1\text{ V}$ . Find the additional resistance which has to be joined with the series in voltmeter to increase the range of voltmeter to  $100\text{ V}$  :-

(1)  $10\ \Omega$  (2)  $\frac{1}{99}\ \Omega$

(3)  $99\ \Omega$  (4)  $100\ \Omega$

**CE0105**

- 102.** A galvanometer having a resistance  $G$  and current  $i_a$  flowing in it, produces full scale deflection. If  $S_1$  is the value of shunt which converts it into an ammeter of range  $0 - i$  and  $S_2$  is the value of the shunt for the range  $0 - 2i$ .

Then the ratio  $\frac{S_1}{S_2}$  will be :-

(1) 1 (2) 2

(3)  $\frac{1}{2} \left( \frac{i - i_a}{2i - i_a} \right)$  (4)  $\left( \frac{2i - i_a}{i - i_a} \right)$

**CE0106**


## POTENTIOMETER

- 103.** It is observed in a potentiometer experiment that no current passes through the galvanometer, when the terminals of a cell are connected across a certain length of the potentiometer wire. On shunting the cell by a  $2\ \Omega$  resistance, the balancing length is reduced to half. The internal resistance of the cell is :-

(1)  $4\ \Omega$  (2)  $2\ \Omega$  (3)  $9\ \Omega$  (4)  $18\ \Omega$

**CE0108**

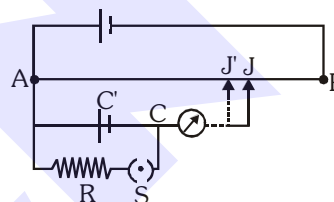- 104.** In the potentiometer circuit shown in the figure, the balancing length  $AJ = 60\text{ cm}$  when switch  $S$  is open. When switch  $S$  is closed and the value of  $R = 5\ \Omega$ , the balancing length  $AJ' = 50\text{ cm}$ . The internal resistance of the cell  $C'$  is :-



(1)  $1.2\ \Omega$  (2)  $1.0\ \Omega$  (3)  $0.8\ \Omega$  (4)  $0.6\ \Omega$

**CE0109**

- 105.** In a potentiometer experiment when terminals of the cell are connected at distance of  $52\text{ cm}$  on the wire, then no current flows through it. When  $5\ \Omega$  shunt resistance is connected across the cell the balancing length is  $40\text{ cm}$ . The internal resistance of the cell (in  $\Omega$ ) is :-

(1) 5 (2)  $\frac{200}{52}$  (3)  $\frac{52}{8}$  (4) 1.5

**CE0110**

- 106.** A potentiometer wire has a resistance  $40\ \Omega$  and its length is  $10\text{ m}$ . It is connected to a resistance of  $760\ \Omega$  in series. If emf of battery is  $2\text{ V}$  then potential gradient is :-

(1)  $0.5 \times 10^{-6}\text{ V/m}$  (2)  $1 \times 10^{-6}\text{ V/m}$   
(3)  $1 \times 10^{-2}\text{ V/m}$  (4)  $2 \times 10^{-6}\text{ V/m}$

**CE0111**

- 107.** A  $6\text{ volts}$  battery is connected to the terminals of a three metres long wire of uniform thickness and  $100\text{ ohm}$  resistance. The potential difference between two points on the wire separated by a distance of  $50\text{ cm}$  will be :-

(1)  $3\text{ volts}$  (2)  $1\text{ volt}$  (3)  $1.5\text{ volts}$  (4)  $2\text{ volts}$

**CE0112**


108. Potentiometer is used for measuring :  
 (1) potential difference (2) current  
 (3) internal resistance (4) All of these

CE0113

109. Length of a potentiometer wire is kept long and uniform to achieve :-  
 (1) uniform and more potential gradient  
 (2) non-uniform and more potential gradient  
 (3) uniform and less potential gradient  
 (4) non-uniform and less potential gradient

CE0114

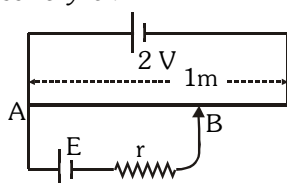
110. In figure battery E is balanced over a 55 cm length of potentiometer wire but when a resistance of  $10\ \Omega$  is connected in parallel with the battery then it balances over a 50 cm length of the potentiometer wire then internal resistance  $r$  of the battery is :-



- (1)  $1\ \Omega$  (2)  $3\ \Omega$  (3)  $10\ \Omega$  (4)  $5\ \Omega$

CE0115

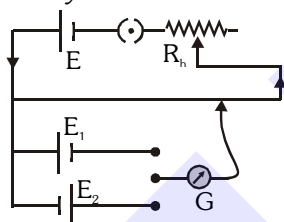
111. The following diagram shows the circuit for the comparison of e.m.f. of two cells. The circuit can be corrected by :-



- (1) reversing the terminals of E  
 (2) reversing the terminals of  $E_1$   
 (3) reversing the terminals of  $E_2$   
 (4) reversing the current in  $R_h$ .

CE0116

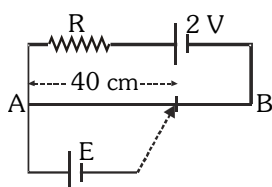
112. AB is a potentiometer wire of length 100 cm and resistance 10 ohms. It is connected in series with a resistance  $R = 40$  ohms and a battery of e.m.f. 2 V and negligible internal resistance. If a source of unknown e.m.f. E is balanced by 40 cm length of the potentiometer wire, the value of E is :-



- (1) 0.8 V (2) 1.6 V  
 (3) 0.08 V (4) 0.16 V

CE0117

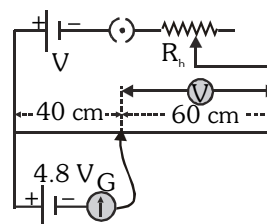
113. In the following circuit, the reading of the voltmeter will be :- (in volts)



- (1) 7.2 (2) 4.8  
 (3) 6 (4) 4

CE0118

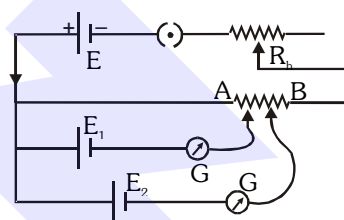
114. In the following diagram, the deflection in the galvanometer in a potentiometer circuit is zero, then :-



- (1)  $E_1 > E_2$  (2)  $E_2 > E_1$   
 (3)  $E_1 = E_2$  (4)  $E_1 + E_2 = E$

CE0119

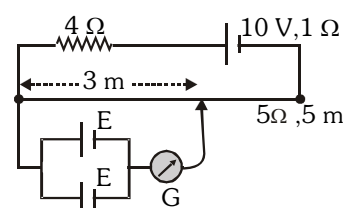115. A resistance of  $4\ \Omega$  and a wire of length 5 m and resistance  $5\ \Omega$  are joined in series and connected to a cell of e.m.f. 10 V and internal resistance  $1\ \Omega$ . A Parallel combination of two identical cells is balanced across 300 cm length of the wire. The e.m.f. E of each cell is :



- (1) 1.5 V (2) 3.0 V  
 (3) 0.67 V (4) 1.33 V

CE0120

116. The emf of a standard cell is balanced over a 150 cm length of a potentiometer wire. When this cell is shunted by a  $2\ \Omega$  resistance, the null point is obtained at 100 cm. The value of internal resistance of the cell is :-

- (1) 0.1 ohms (2) 1 ohms  
 (3) 2 ohms (4) 0.5 ohms

CE0121



- 117.** The sensitivity of a potentiometer is increased by
- (1) increasing the emf of the cell.
  - (2) increasing the length of the potentiometer wire
  - (3) decreasing the length of the potentiometer wire
  - (4) none of the above.

**CE0122**

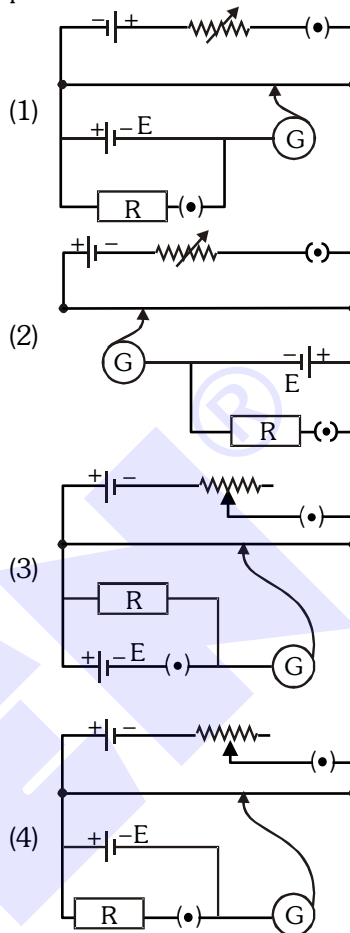
- 118.** A potential gradient is established in the wire by a standard cell for the comparison of emf's of two cells in a potentiometer experiment. Which possibility of the following will lead to the failure of the experiment ?
- (1) the emf of the standard cell is higher than that of the other cells.
  - (2) the diameter of the wire is equal along its length
  - (3) the number of wires is ten.
  - (4) the emf of the standard cell is less than that of either cells

**CE0123**

- 119.** Potentiometer wire length is 10 m, having a total resistance of  $10\ \Omega$ . If a battery of emf 2 volts (of negligible internal resistance) and a rheostat are connected to it then the potential gradient is 20 mV/m; find the resistance imparted through the rheostat :-
- (1)  $90\ \Omega$
  - (2)  $990\ \Omega$
  - (3)  $40\ \Omega$
  - (4)  $190\ \Omega$

**CE0124**

- 120.** The correct circuit for the determination of internal resistance of a battery by using potentiometer is :


**CE0125**
**EXERCISE-I (Conceptual Questions)**
**ANSWER KEY**

Que.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Ans.	2	2	2	3	2	2	3	2	2	3	4	3	3	3	2
Que.	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
Ans.	1	4	4	3	1	3	4	1	2	4	4	3	1	4	3
Que.	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
Ans.	3	3	3	1	2	4	3	4	3	1	1	4	3	1	1
Que.	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
Ans.	1	4	1	1	4	2	1	3	2	2	4	1	2	2	3
Que.	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
Ans.	2	3	3	1	4	1	2	4	2	2	4	3	2	2	3
Que.	76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
Ans.	2	1	4	1	1	1	1	3	2	4	4	2	3	1	1
Que.	91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
Ans.	4	1	1	2	1	3	2	1	2	1	3	4	2	2	4
Que.	106	107	108	109	110	111	112	113	114	115	116	117	118	119	120
Ans.	3	2	4	3	1	3	4	1	2	2	2	2	4	1	4




## EXERCISE-II (Previous Year Questions)

## AIPMT/NEET

## AIPMT 2006

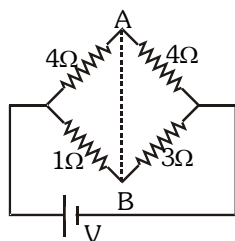1. In the circuit shown, if a conducting wire is connected between points A and B, the current in this wire will :-



- (1) flow from A to B  
 (2) flow in the direction which will be decided by the value of V  
 (3) be zero  
 (4) flow from B to A

CE0126


## AIPMT 2007

2. The resistance of an ammeter is  $13\ \Omega$  and its scale is graduated for currents upto 100 A. After an additional shunt is connected to this ammeter it becomes possible to measure currents upto 750 amperes by this meter. The value of shunt-resistance is :-
- (1) 2 k $\Omega$     (2) 20  $\Omega$     (3) 2  $\Omega$     (4) 0.2  $\Omega$

CE0128

## AIPMT 2008

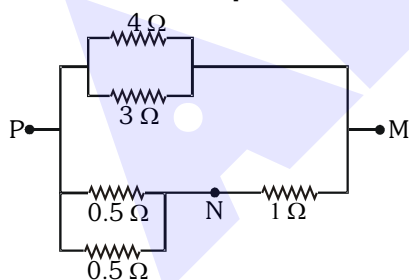3. In the circuit shown, the current through the  $4\ \Omega$  resistor is 1 A when the points P and M are connected to a d.c. voltage source. The potential difference between the points M and N is :-



- (1) 0.5 volts    (2) 3.2 volts  
 (3) 1.5 volts    (4) 1.0 volt


CE0129

4. A galvanometer of resistance  $50\ \Omega$  is connected to a battery of 3 V along with a resistance of  $2950\ \Omega$  in series. A full scale deflection of 30 divisions is obtained in the galvanometer. In order to reduce this deflection to 20 divisions, the resistance in series should be :-

- (1) 6050  $\Omega$     (2) 4450  $\Omega$   
 (3) 5050  $\Omega$     (4) 5550  $\Omega$

CE0130

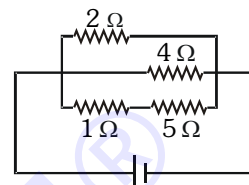5. A current of 3 amperes flows through the  $2\ \Omega$  resistor shown in the circuit. The power dissipated in the  $5\ \Omega$  resistor is :-




- (1) 1 watt    (2) 5 watts  
 (3) 4 watts    (4) 2 watts

CE0131

## AIPMT 2009

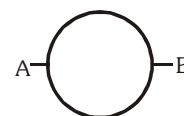
6. A wire of resistance 12 ohms per meter is bent to form a complete circle of radius 10 cm. The resistance between its two diametrically opposite points, A and B as shown in the figure, is :-



- (1) 6  $\Omega$     (2)  $0.6\pi\ \Omega$   
 (3) 3  $\Omega$     (4)  $6\pi\ \Omega$

CE0132

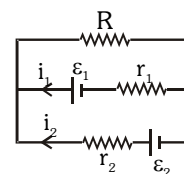7. See the electrical circuit shown in this figure. Which of the following equations is the correct equation for it ?



- (1)  $\varepsilon_1 - (i_1 + i_2)R + i_1 r_1 = 0$   
 (2)  $\varepsilon_1 - (i_1 + i_2)R - i_1 r_1 = 0$   
 (3)  $\varepsilon_2 - i_2 r_2 - \varepsilon_1 - i_1 r_1 = 0$   
 (4)  $-\varepsilon_2 - (i_1 + i_2)R + i_2 r_2 = 0$

CE0133

8. A galvanometer having a coil resistance of  $60\ \Omega$  shows full scale deflection when a current of  $1.0\text{ A}$  passes through it. It can be converted into an ammeter to read currents upto  $5.0\text{ A}$  by :-
- (1) putting in parallel a resistance of  $15\ \Omega$
  - (2) putting in parallel a resistance of  $240\ \Omega$
  - (3) putting in series a resistance of  $15\ \Omega$
  - (4) putting in series a resistance of  $240\ \Omega$

**CE0134**


9. A student measures the terminal potential difference ( $V$ ) of a cell (of emf  $\varepsilon$  and internal resistance  $r$ ) as a function of the current ( $I$ ) flowing through it. The slope and intercept of the graph between  $V$  and  $I$ , then respectively, are :-

- (1)  $-\varepsilon$  and  $r$
- (2)  $\varepsilon$  and  $-r$
- (3)  $-r$  and  $\varepsilon$
- (4)  $r$  and  $-\varepsilon$

**CE0135**

**AIPMT (Pre) 2010**

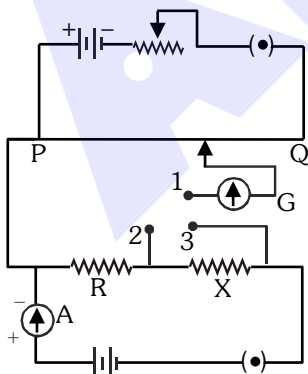10. A potentiometer circuit is set up as shown. The potential gradient, across the potentiometer wire, is  $k$  volts/cm and the ammeter, present in the circuit, reads  $1.0\text{ A}$  when two way key is switched off. The balance points, when the key between the terminals (i) 1 and 2 (ii) 1 and 3, is plugged in, are found to be at lengths  $\ell_1$  cm and  $\ell_2$  cm respectively. The magnitudes, of the resistors  $R$  and  $X$ , (in ohms), are then, equal to respectively :-



- (1)  $k\ell_1$  and  $k\ell_2$
- (2)  $k(\ell_2 - \ell_1)$  and  $k\ell_2$
- (3)  $k\ell_1$  and  $k(\ell_2 - \ell_1)$
- (4)  $k(\ell_2 - \ell_1)$  and  $k\ell_1$

**CE0136**

11. A galvanometer has a coil of resistance  $100\ \Omega$  and gives full scale deflection for  $30\text{ mA}$  current. If it is to work as a voltmeter of  $30\text{ V}$  range, the resistance required to be added will be:-

- (1)  $1000\ \Omega$
- (2)  $900\ \Omega$
- (3)  $1800\ \Omega$
- (4)  $500\ \Omega$

**CE0137**

12. Consider the following two statements :

- (A) Kirchhoff's junction law follows from the conservation of charge.
- (B) Kirchhoff's loop law follows from the conservation of energy.

Which of the following is correct ?

- (1) Both (A) and (B) are correct
- (2) Both (A) and (B) are wrong
- (3) (A) is correct and (B) is wrong
- (4) (A) is wrong and (B) is correct.

**CE0138**


**AIPMT (Pre) 2011**

13. A current of  $2\text{ A}$  flows through a  $2\ \Omega$  resistor when connected across a battery. The same battery supplies a current of  $0.5\text{ A}$  when connected across a  $9\ \Omega$  resistor. The internal resistance of the battery is :-

- (1)  $0.5\ \Omega$
- (2)  $1/3\ \Omega$
- (3)  $1/4\ \Omega$
- (4)  $1\ \Omega$

**CE0139**

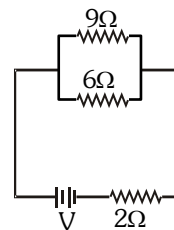14. If power dissipated in the  $9\ \Omega$  resistor in the circuit shown is  $36\text{ Watt}$ , the potential difference across the  $2\ \Omega$  resistor is :-




- (1)  $4\text{ V}$
- (2)  $8\text{ V}$
- (3)  $10\text{ V}$
- (4)  $2\text{ V}$

**CE0140**

**AIPMT (Mains) 2011**

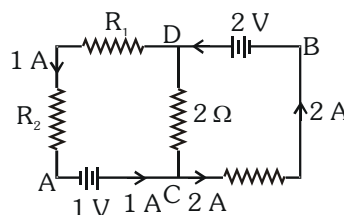15. In the circuit shown in the figure, if the potential at point A is taken to be zero, the potential at point B is :-



- (1)  $+1\text{ V}$
- (2)  $-1\text{ V}$
- (3)  $+2\text{ V}$
- (4)  $-2\text{ V}$

**CE0141**

16. A galvanometer of resistance,  $G$ , is shunted by a resistance  $S$ . To keep the main current in the circuit unchanged, the resistance to be put in series with the arrangement is :-


(1)  $\frac{G}{(S+G)}$  (2)  $\frac{S^2}{(S+G)}$   
 (3)  $\frac{SG}{(S+G)}$  (4)  $\frac{G^2}{(S+G)}$

CE0142

## AIPMT (Pre) 2012

17. A ring is made of a wire having a resistance  $R_0 = 12 \Omega$ . Find the points A and B as shown in the figure at which a current carrying conductor should be connected so that the resistance  $R$  of the sub circuit between these points is equal to  $\frac{8}{3} \Omega$  :-

(1)  $\frac{\ell_1}{\ell_2} = \frac{3}{8}$   
 (2)  $\frac{\ell_1}{\ell_2} = \frac{1}{2}$   
 (3)  $\frac{\ell_1}{\ell_2} = \frac{5}{8}$   
 (4)  $\frac{\ell_1}{\ell_2} = \frac{1}{3}$

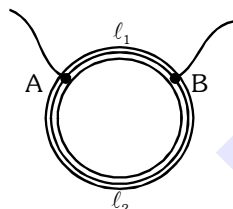


CE0143

18. If voltage across a bulb rated 220 volts 100 watts drops by 2.5% of its rated value, the percentage of the rated value by which the power would decrease is :-

(1) 5% (2) 10% (3) 20% (4) 2.5%

CE0144

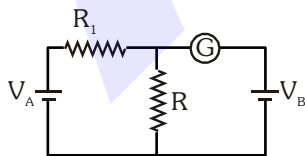19. In the circuit shown the cells A and B have negligible resistances. For  $V_A = 12 \text{ V}$ ,  $R_1 = 500 \Omega$  and  $R = 100 \Omega$  the galvanometer (G) shows no deflection. The value of  $V_B$  is :-



(1) 12 V (2) 6 V (3) 4 V (4) 2 V

CE0145


20. A millivoltmeter of 25 millivolts range is to be converted into an ammeter of 25 amperes range. The value (in ohms) of necessary shunt will be :

(1) 1 (2) 0.05 (3) 0.001 (4) 0.01

CE0146

## AIPMT (Mains) 2012

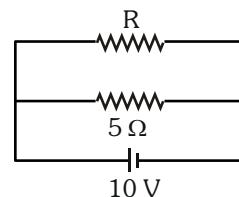
21. The power dissipated in the circuit shown in the figure is 30 watts. The value of  $R$  is :-



(1) 10  $\Omega$  (2) 30  $\Omega$  (3) 20  $\Omega$  (4) 15  $\Omega$

CE0147

22. A cell having an emf  $\varepsilon$  and internal resistance  $r$  is connected across a variable external resistance  $R$ . As the resistance  $R$  is increased, the plot of potential difference  $V$  across  $R$  is given by :-

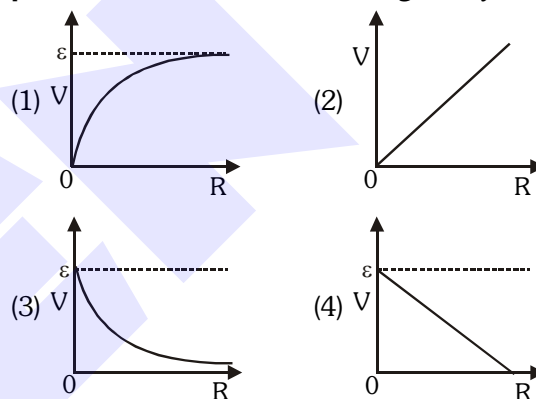

CE0148

## NEET-UG 2013

23. A wire of resistance  $4 \Omega$  is stretched to twice its original length. The resistance of the stretched wire would be :-

(1) 16  $\Omega$  (2) 2  $\Omega$  (3) 4  $\Omega$  (4) 8  $\Omega$

CE0151

24. The internal resistance of a 2.1 V cell which gives a current of 0.2 A through a resistance of  $10 \Omega$  is :-

(1) 1.0  $\Omega$  (2) 0.2  $\Omega$  (3) 0.5  $\Omega$  (4) 0.8  $\Omega$

CE0152

25. The resistances of the four arms P, Q, R and S in a Wheatstone bridge are 10 ohms, 30 ohms, 30 ohms and 90 ohms, respectively. The e.m.f. and internal resistance of the cell are 7 volts and 5 ohms respectively. If the galvanometer resistance is 50 ohms, the current drawn from the cell will be :-

(1) 2.0 A (2) 1.0 A (3) 0.2 A (4) 0.1 A

CE0153


**AIPMT 2014**

- 26.** Two cities are 150 km apart. Electric power is sent from one city to another city through copper wires. The fall of potential per km is 8 volts and the average resistance per km is  $0.5 \Omega$ . the power loss in the wires is :-

- (1) 19.2 W (2) 19.2 kW  
(3) 19.2 J (4) 12.2 kW

**CE0155**

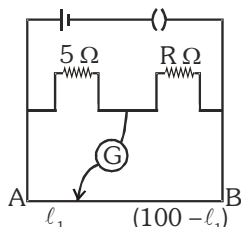- 27.** The resistance in the two arms of a meter bridge are  $5 \Omega$  and  $R \Omega$ , respectively. When the resistance  $R$  is shunted with an equal resistance, the new balance point is at  $1.6 \ell_1$ . The resistance 'R' is :-



- (1) 10  $\Omega$  (2) 15  $\Omega$  (3) 20  $\Omega$  (4) 25  $\Omega$

**CE0156**

- 28.** A potentiometer circuit has been set up for finding the internal resistance of a given cell. The main battery, used across the potentiometer wire, has an emf of 2.0 V and a negligible internal resistance. The potentiometer wire itself is 4m long, When a resistance  $R$ , connected across the given cell, has values of,

- (i) infinity (ii) 9.5  $\Omega$

The balancing lengths on the potentiometer wire are found to be 3 m and 2.85 m respectively. The value of internal resistance of the cell is :-

- (1) 0.25  $\Omega$  (2) 0.95  $\Omega$   
(3) 0.5  $\Omega$  (4) 0.75  $\Omega$

**CE0157**

- 29.** In an ammeter 0.2% of main current passes through the galvanometer. If resistance of galvanometer is  $G$ , then resistance of ammeter will be :-

- (1)  $\frac{1}{499} G$  (2)  $\frac{499}{500} G$   
(3)  $\frac{1}{500} G$  (4)  $\frac{500}{499} G$

**CE0158**

**Re-AIPMT 2015**

- 30.** A potentiometer wire of length  $L$  and resistance  $r$  is connected in series with a battery of e.m.f.  $E_0$  and a resistance  $r_1$ . An unknown e.m.f.  $E$  is balanced at a length  $\ell$  of the potentiometer wire.

The e.m.f.  $E$  will be given by :

- (1)  $\frac{LE_0 r}{(r + r_1) \ell}$  (2)  $\frac{LE_0 r}{\ell r_1}$   
(3)  $\frac{E_0 r}{(r + r_1)} \cdot \frac{\ell}{L}$  (4)  $\frac{E_0 \ell}{L}$

**CE0159**

- 31.** Two metal wires of identical dimensions are connected in series. If  $\sigma_1$  and  $\sigma_2$  are the conductivities of the metal wires respectively, the effective conductivity of the combination is :-

- (1)  $\frac{\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$  (2)  $\frac{2\sigma_1 \sigma_2}{\sigma_1 + \sigma_2}$   
(3)  $\frac{\sigma_1 + \sigma_2}{2\sigma_1 \sigma_2}$  (4)  $\frac{\sigma_1 + \sigma_2}{\sigma_1 \sigma_2}$

**CE0160**

- 32.** A circuit contains an ammeter, a battery of 30 V and a resistance 40.8 ohm all connected in series. If the ammeter has a coil of resistance 480 ohm and a shunt of 20 ohm, the reading in the ammeter will be :-

- (1) 1 A (2) 0.5 A  
(3) 0.25 A (4) 2 A

**CE0161**

**AIPMT - 2015**

- 33.** Across a metallic conductor of non-uniform cross section a constant potential difference is applied. The quantity which remains constant along the conductor is :

- (1) current  
(2) drift velocity  
(3) electric field  
(4) current density


**CE0162**

34. A potentiometer wire has length 4 m and resistance  $8\Omega$ . The resistance that must be connected in series with the wire and an accumulator of e.m.f. 2V, so as to get a potential gradient 1 mV per cm on the wire is :

(1)  $40\Omega$  (2)  $44\Omega$  (3)  $48\Omega$  (4)  $32\Omega$

CE0163

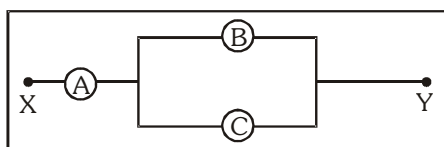35. A, B and C are voltmeters of resistance R,  $1.5R$  and  $3R$  respectively as shown in the figure. When some potential difference is applied between X and Y, the voltmeter readings are  $V_A$ ,  $V_B$  and  $V_C$  respectively. Then :



- (1)  $V_A \neq V_B = V_C$  (2)  $V_A = V_B \neq V_C$   
 (3)  $V_A \neq V_B \neq V_C$  (4)  $V_A = V_B = V_C$

CE0164

## NEET-I 2016


36. A potentiometer wire is 100 cm long and a constant potential difference is maintained across it. Two cells are connected in series first to support one another and then in opposite direction. The balance points are obtained at 50 cm and 10 cm from the positive end of the wire in the two cases. The ratio of emf's is :-

(1) 5 : 1 (2) 5 : 4 (3) 3 : 4 (4) 3 : 2

CE0167

## NEET-II 2016

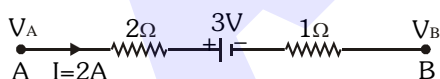37. The potential difference ( $V_A - V_B$ ) between the points A and B in the given figure is :-



- (1) + 6 V (2) + 9 V  
 (3) - 3 V (4) + 3 V

CE0168

38. A filament bulb (500 W, 100 V) is to be used in a 230 V main supply. When a resistance R is connected in series, it works perfectly and the bulb consumes 500 W. The value of R is :-

(1)  $26\Omega$  (2)  $13\Omega$   
 (3)  $230\Omega$  (4)  $46\Omega$

CE0169

## NEET(UG)-2017

39. The resistance of a wire is 'R' ohm. If it is melted and stretched to 'n' times its original length, its new resistance will be :-

(1)  $\frac{R}{n}$  (2)  $n^2R$  (3)  $\frac{R}{n^2}$  (4)  $nR$

CE0173

40. A potentiometer is an accurate and versatile device to make electrical measurements of E.M.F. because the method involves :-

- (1) Potential gradients  
 (2) A condition of no current flow through the galvanometer  
 (3) A combination of cells, galvanometer and resistances  
 (4) Cells

CE0174


## NEET(UG)-2018

41. A set of 'n' equal resistors, of value 'R' each, are connected in series to a battery of emf 'E' and internal resistance 'R'. The current drawn is I. Now, the 'n' resistors are connected in parallel to the same battery. Then the current drawn from battery becomes 10 I. The value of 'n' is :-

(1) 10 (2) 11 (3) 20 (4) 9

CE0177

42. A battery consists of a variable number 'n' of identical cells (having internal resistance 'r' each) which are connected in series. The terminals of the battery are short-circuited and the current I is measured. Which of the graphs shows the correct relationship between I and n ?

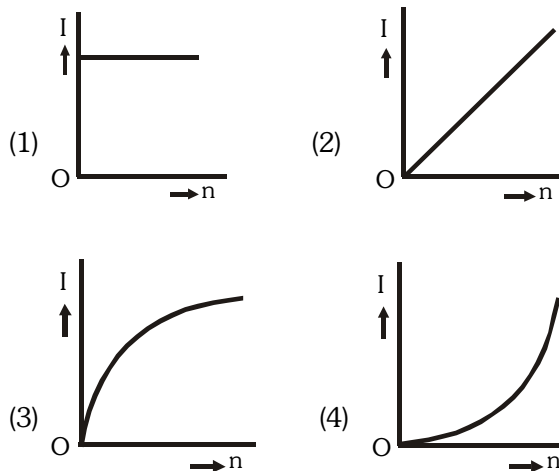

CE0178

43. A carbon resistor ( $47 \pm 4.7$ ) k $\Omega$  is to be marked with rings of different colours for its identification. The colour code sequence will be :-  
 (1) Violet – Yellow – Orange – Silver  
 (2) Yellow – Violet – Orange – Silver  
 (3) Yellow – Green – Violet – Gold  
 (4) Green – Orange – Violet – Gold


**CE0179**

44. Current sensitivity of a moving coil galvanometer is 5 div/mA and its voltage sensitivity (angular deflection per unit voltage applied) is 20 div/V. The resistance of the galvanometer is  
 (1) 40  $\Omega$  (2) 25  $\Omega$  (3) 250  $\Omega$  (4) 500  $\Omega$

**CE0180**

**NEET(UG)-2019**

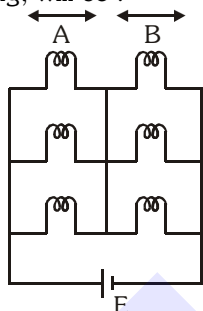45. Six similar bulbs are connected as shown in the figure with a DC source of emf  $E$ , and zero internal resistance. The ratio of power consumption by the bulbs when (i) all are glowing and (ii) in the situation when two from section A and one from section B are glowing, will be :




- (1) 4 : 9 (2) 9 : 4 (3) 1 : 2 (4) 2 : 1

**CE0247**

46. Which of the following acts as a circuit protection device?  
 (1) conductor (2) inductor  
 (3) switch (4) fuse

**CE0248**

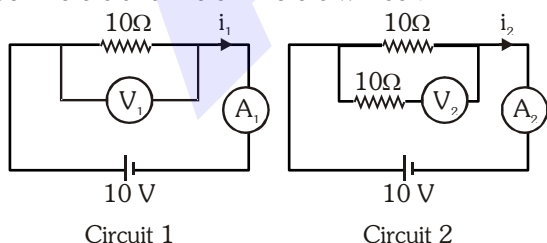47. In the circuits shown below, the readings of the voltmeters and the ammeters will be :




- Circuit 1  
 (1)  $V_2 > V_1$  and  $i_1 = i_2$   
 (2)  $V_1 = V_2$  and  $i_1 > i_2$   
 (3)  $V_1 = V_2$  and  $i_1 = i_2$   
 (4)  $V_2 > V_1$  and  $i_1 > i_2$

Circuit 2

**CE0249**

**NEET(UG)-2019 (Odisha)**

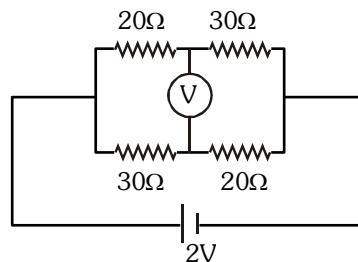
48. The reading of an ideal voltmeter in the circuit shown is :



- (1) 0.6 V (2) 0 V (3) 0.5 V (4) 0.4 V

**CE0250**

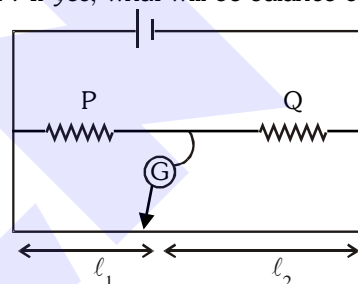49. The metre bridge shown is in balanced position with  $\frac{P}{Q} = \frac{\ell_1}{\ell_2}$ . If we now interchange the positions of galvanometer and cell, will the bridge work? If yes, what will be balance condition?



- (1) yes,  $\frac{P}{Q} = \frac{\ell_2 - \ell_1}{\ell_2 + \ell_1}$  (2) no, no null point  
 (3) yes,  $\frac{P}{Q} = \frac{\ell_2}{\ell_1}$  (4) yes,  $\frac{P}{Q} = \frac{\ell_1}{\ell_2}$

**CE0251**

**NEET(UG)-2020**

50. The color code of a resistance is given below



The values of resistance and tolerance, respectively, are :

- (1) 470  $\Omega$ , 5% (2) 470 k $\Omega$ , 5%  
 (3) 47 k $\Omega$ , 10% (4) 4.7 k $\Omega$ , 5%

**CE0252**


51. A charged particle having drift velocity of  $7.5 \times 10^{-4} \text{ ms}^{-1}$  is in an electric field of  $3 \times 10^{-10} \text{ Vm}^{-1}$ , has a mobility in  $\text{m}^2 \text{ V}^{-1} \text{ s}^{-1}$  of :

- (1)  $2.25 \times 10^{-15}$  (2)  $2.25 \times 10^{15}$   
 (3)  $2.5 \times 10^6$  (4)  $2.5 \times 10^{-6}$

**CE0253**



52. Which of the following graph represents the variation of resistivity ( $\rho$ ) with temperature ( $T$ ) for copper ?

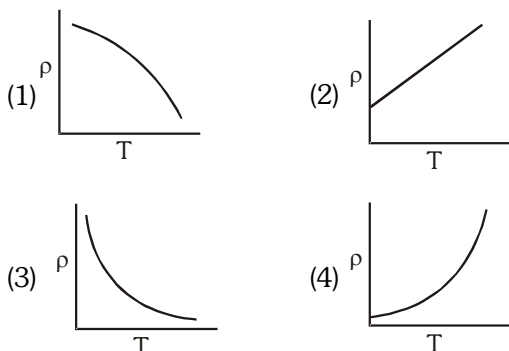


CE0254

53. A resistance wire connected in the left gap of a metre bridge balances a  $10\ \Omega$  resistance in the right gap at a point which divides the bridge wire in the ratio 3 : 2. If the length of the resistance wire is 1.5 m, then the length of  $1\ \Omega$  of the resistance wire is :
- (1)  $1.5 \times 10^{-2}$  m (2)  $1.0 \times 10^{-2}$  m  
 (3)  $1.0 \times 10^{-1}$  m (4)  $1.5 \times 10^{-1}$  m

CE0255

## NEET(UG)-2020 (Covid-19)

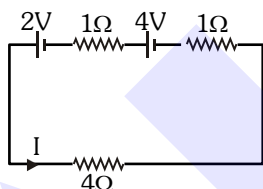
54. For the circuit shown in the figure, the current  $I$  will be



- (1) 0.75 A (2) 1 A  
 (3) 1.5 A (4) 0.5 A

CE0256

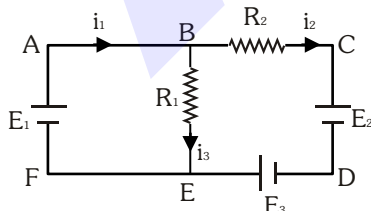
55. For the circuit given below, the Kirchoff's loop rule for the loop BCDEB is given by the equation



- (1)  $-i_2R_2 + E_2 - E_3 + i_3R_1 = 0$   
 (2)  $i_2R_2 + E_2 - E_3 - i_3R_1 = 0$   
 (3)  $i_2R_2 + E_2 + E_3 + i_3R_1 = 0$   
 (4)  $-i_2R_2 + E_2 + E_3 + i_3R_1 = 0$

CE0257

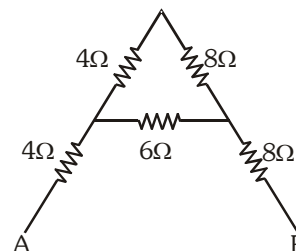56. The equivalent resistance between A and B for the mesh shown in the figure is



- (1)  $7.2\ \Omega$  (2)  $16\ \Omega$   
 (3)  $30\ \Omega$  (4)  $4.8\ \Omega$

CE0258

57. Two solid conductors are made up of same material, have same length and same resistance. One of them has a circular cross section of area  $A_1$  and the other one has a square cross section of area  $A_2$ . The ratio  $A_1/A_2$  is

- (1) 1.5 (2) 1  
 (3) 0.8 (4) 2

CE0259

## NEET(UG)-2021

58. **Column-I** gives certain physical terms associated with flow of current through a metallic conductor. **Column-II** gives some mathematical relations involving electrical quantities. Match **Column-I** and **Column-II** with appropriate relations.

Column-I		Column-II	
(A)	Drift Velocity	(P)	$\frac{m}{ne^2\rho}$
(B)	Electrical Resistivity	(Q)	$nev_d$
(C)	Relaxation Period	(R)	$\frac{eE}{m}\tau$
(D)	Current Density	(S)	$\frac{E}{J}$

- (1) (A)-(R), (B)-(S), (C)-(P), (D)-(Q)  
 (2) (A)-(R), (B)-(S), (C)-(Q), (D)-(P)  
 (3) (A)-(R), (B)-(P), (C)-(S), (D)-(Q)  
 (4) (A)-(R), (B)-(Q), (C)-(S), (D)-(P)

CE0260



59. The effective resistance of a parallel connection that consists of four wires of equal length, equal area of cross-section and same material is  $0.25 \Omega$ . What will be the effective resistance if they are connected in series ?

(1)  $0.25 \Omega$  (2)  $0.5 \Omega$   
(3)  $1 \Omega$  (4)  $4 \Omega$


**CE0261**

60. In a potentiometer circuit a cell of EMF  $1.5 \text{ V}$  gives balance point at  $36 \text{ cm}$  length of wire. If another cell of EMF  $2.5 \text{ V}$  replaces the first cell, then at what length of the wire, the balance point occurs?

(1)  $60 \text{ cm}$  (2)  $21.6 \text{ cm}$   
(3)  $64 \text{ cm}$  (4)  $62 \text{ cm}$

**CE0262**

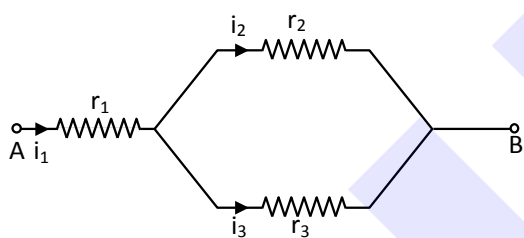61. Three resistors having resistances  $r_1$ ,  $r_2$  and  $r_3$  are connected as shown in the given circuit. The ratio  $\frac{i_3}{i_1}$  of currents in terms of resistances used in the circuit is :




(1)  $\frac{r_1}{r_2 + r_3}$  (2)  $\frac{r_2}{r_2 + r_3}$   
(3)  $\frac{r_1}{r_1 + r_2}$  (4)  $\frac{r_2}{r_1 + r_3}$

**CE0263**

**NEET(UG)-2021 (Paper-2)**

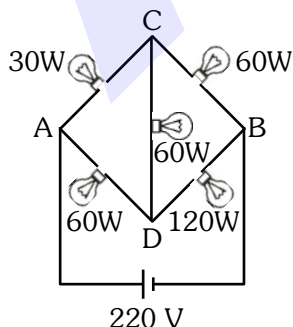
62. Five bulbs each have same voltage rating  $220 \text{ V}$  are connected as shown in the figure. The total power consumed in the circuit is



(1)  $20 \text{ W}$  (2)  $40 \text{ W}$  (3)  $60 \text{ W}$  (4)  $100 \text{ W}$

**CE0264**

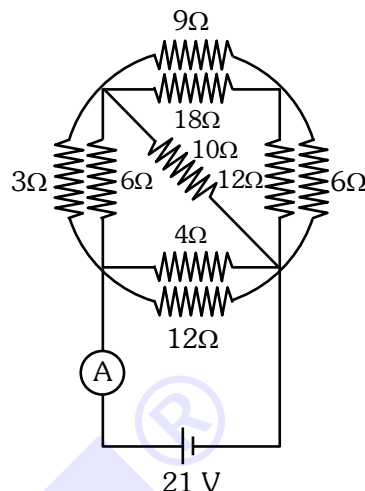63. In the circuit as shown, the reading of ideal ammeter is



(1)  $5 \text{ A}$  (2)  $8 \text{ A}$  (3)  $9 \text{ A}$  (4)  $10 \text{ A}$

**CE0265**

64. Kirchhoff's voltage law is based on the conservation of

(1) Charge (2) Energy  
(3) Momentum (4) Current

**CE0266**

**NEET(UG)-2022**

65. Two resistors of resistance,  $100 \Omega$  and  $200 \Omega$  are connected in parallel in an electrical circuit. The ratio of the thermal energy developed in  $100 \Omega$  to that in  $200 \Omega$  in a given time is :

(1)  $2 : 1$  (2)  $1 : 4$   
(3)  $4 : 1$  (4)  $1 : 2$

**CE0267**

66. As the temperature increase, the electrical resistance :

(1) decreases for both conductors and semiconductors  
(2) increases for conductors but decreases for semiconductors  
(3) decreases for conductors but increase for semiconductors  
(4) increases for both conductors and semiconductors.

**CE0268**


67. A copper wire of length 10 m and radius  $(10^{-2} / \sqrt{\pi})$  m has electrical resistance of  $10 \Omega$ .

The current density in the wire for an electric field strength of 10 (V/m) is:

- (1)  $10^6 \text{ A/m}^2$  (2)  $10^{-5} \text{ A/m}^2$   
(3)  $10^5 \text{ A/m}^2$  (4)  $10^4 \text{ A/m}^2$

CE0269

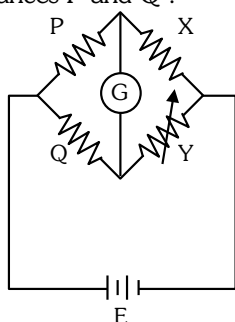68. A wheatstone bridge is used to determine the value of unknown resistance X by adjusting the variable resistance Y as shown in the figure. For the most precise measurement of X, the resistances P and Q :




- (1) should be approximately equal and are small  
(2) should be very large and unequal  
(3) do not play any significant role  
(4) should be approximately equal to  $2X$

CE0270

NEET(UG)-2022 (Overseas)

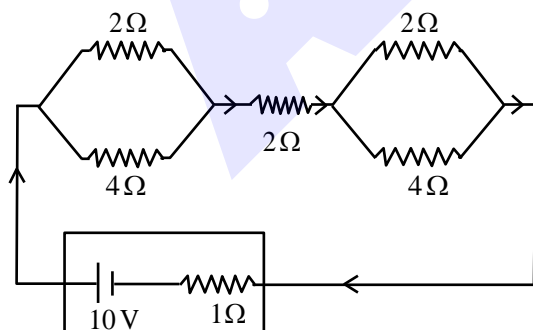
69. A network of resistors is connected across a 10 V battery with internal resistance of  $1 \Omega$  as shown in the circuit diagram. The equivalent resistance of the circuit is:



- (1)  $\frac{14}{3} \Omega$  (2)  $\frac{12}{7} \Omega$   
(3)  $\frac{14}{7} \Omega$  (4)  $\frac{17}{3} \Omega$


CE0271

70. The plot of current I flowing through a conductor versus the applied voltage V across the ends of a conductor is:

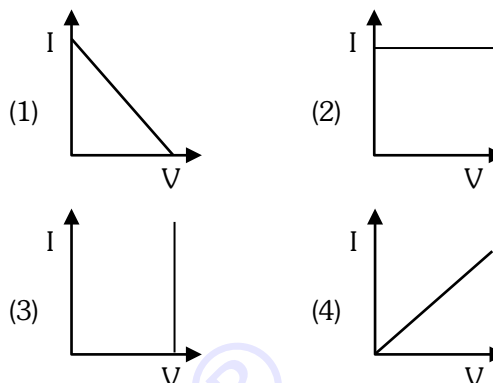

CE0272

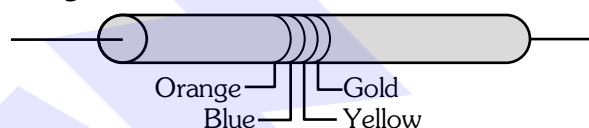
71. The value of resistance for the colour code of the given resistor is:



- (1)  $(470 \pm 47) \text{ k}\Omega$   
(2)  $(360 \pm 36) \text{ k}\Omega$   
(3)  $(360 \pm 18) \text{ k}\Omega$   
(4)  $(36 \pm 36) \text{ k}\Omega$

CE0273

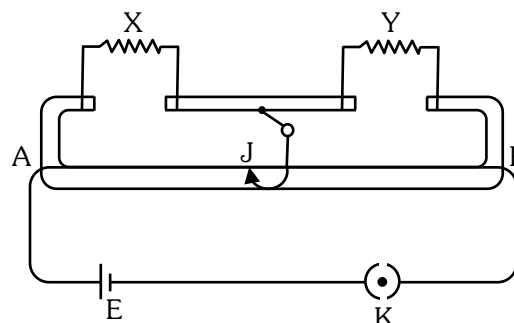72. In a metre bridge experiment, the null point is at a distance of 30 cm from A. If a resistance of  $16 \Omega$  is connected in parallel with resistance Y, the null point occurs at 50 cm from A. The value of the resistance Y is:



- (1)  $\frac{40}{3} \Omega$  (2)  $\frac{64}{3} \Omega$   
(3)  $\frac{48}{3} \Omega$  (4)  $\frac{112}{3} \Omega$

CE0274


**Re-NEET(UG)-2022**

- 73.** A cell of emf 4 V and internal resistance  $0.5 \Omega$  is connected to a  $7.5 \Omega$  external resistance. The terminal potential difference of the cell is :-

(1) 3.75 V (2) 4.25 V  
(3) 4 V (4) 0.375 V

**CE0275**

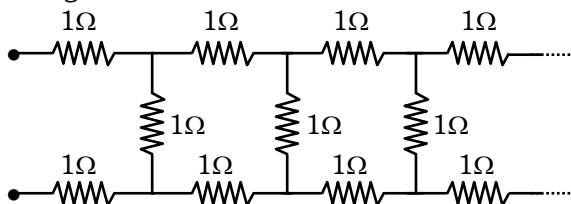- 74.** The equivalent resistance of the infinite network given below is :



(1)  $2 \Omega$  (2)  $(1 + \sqrt{2}) \Omega$   
(3)  $(1 + \sqrt{3}) \Omega$  (4)  $(1 + \sqrt{5}) \Omega$


**CE0276**

- 75.** The reciprocal of resistance is :

(1) reactance  
(2) mobility  
(3) conductivity  
(4) conductance

**CE0277**

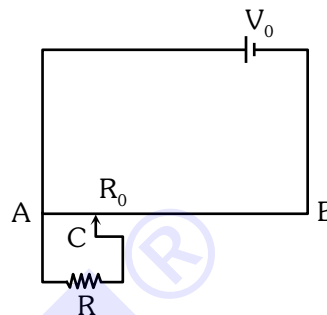- 76.** The sliding contact C is at one fourth of the length of the potentiometer wire (AB) from A as shown in the circuit diagram. If the resistance of the wire AB is  $R_0$ , then the potential drop (V) across the resistor R is:



(1)  $\frac{4V_0 R}{3R_0 + 16R}$  (2)  $\frac{4V_0 R}{3R_0 + R}$   
(3)  $\frac{2V_0 R}{4R_0 + R}$  (4)  $\frac{2V_0 R}{2R_0 + 3R}$

**CE0278**
**EXERCISE-II (Previous Year Questions)**
**ANSWER KEY**

Que.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Ans.	4	3	2	2	2	2	2	1	3	3	2	1	2	3	1
Que.	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
Ans.	4	2	1	4	3	1	1	1	3	3	2	2	3	3	3
Que.	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
Ans.	2	2	1	4	4	4	2	1	2	2	1	1	2	3	2
Que.	46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
Ans.	4	3	4	4	1	3	4	3	2	2	2	2	1	4	1
Que.	61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
Ans.	2	3	4	2	1	2	3	1	4	4	3	2	1	3	4
Que.	76														
Ans.	1														

## EXERCISE-III (Analytical Questions)


## Master Your Understanding

1. When a potential difference is applied across the ends of a linear metallic conductor :-

- (1) group of free electrons are accelerated continuously from the lower potential end to the higher potential end of the conductor
- (2) group of free electrons are accelerated continuously from the higher potential end to the lower potential end of the conductor
- (3) group of free electrons acquire a constant drift velocity from the lower potential end to the higher potential end of the conductor.
- (4) each free electron is set in motion from their position of rest.

CE0186

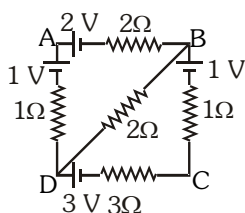
2. In the circuit shown in figure, cells of emf 2, 1, 3 and 1 V, respectively having resistances  $2\ \Omega$ ,  $1\ \Omega$ ,  $3\ \Omega$  and  $1\ \Omega$  are their internal resistances respectively. The potential difference between D and B. (in volts)



- (1)  $\frac{5}{13}$       (2)  $\frac{2}{13}$       (3)  $\frac{10}{13}$       (4)  $\frac{7}{13}$

CE0189

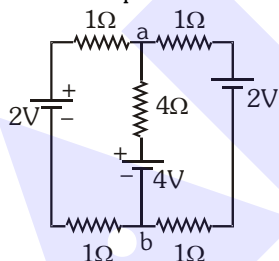
3. For the circuit shown in figure, the potential difference between points a and b is :-



- (1) 2.4 V      (2) 2.8 V      (3) 2 V      (4) 3.2 V

CE0190

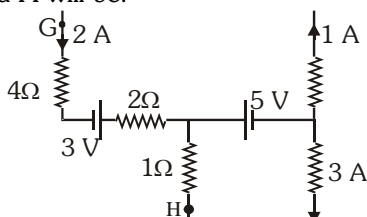
4. In the part of a circuit shown in figure, the potential difference ( $V_G - V_H$ ) between points G and H will be:-



- (1) 0      (2) 15 V      (3) 7 V      (4) 3 V

CE0191

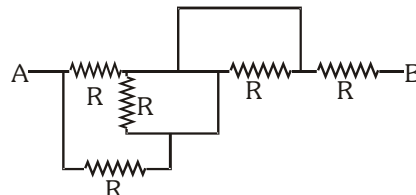
5. What is the equivalent resistance between A and B ?



- (1)  $\frac{3R}{2}$       (2)  $2R$       (3)  $R$       (4)  $\frac{R}{2}$

CE0192

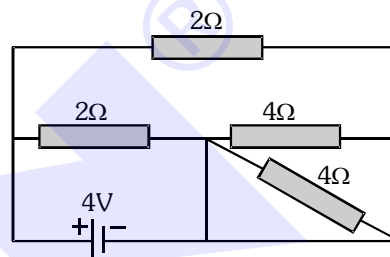
6. Electric current through the battery is :-



- (1) 4 A      (2) 3 A      (3) 2 A      (4) 0 A

CE0193

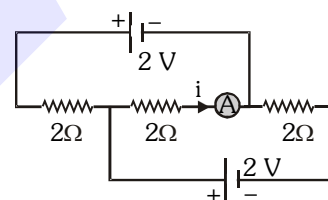7. Reading of ammeter for the following circuit is :-



- (1) 1 A      (2)  $\frac{1}{2}$  A      (3)  $\frac{2}{3}$  A      (4) 3 A

CE0194

8. 100 cells, each of e.m.f. 5 V and internal resistance  $1\ \Omega$ , are to be arranged so as to drive maximum current in a  $25\ \Omega$  resistance. Each row is to contain equal number of cells. The number of rows should be :-

- (1) 2      (2) 4      (3) 5      (4) 10


CE0195

9. Two nonideal batteries are connected in parallel; consider the following statements :

- (A) The equivalent emf is smaller than either of the two emfs.
  - (B) The equivalent internal resistance is smaller than either of the two internal resistances.
- (1) both A and B are correct  
 (2) A is correct but B is wrong  
 (3) B is correct but A is wrong  
 (4) both A and B are wrong

CE0196

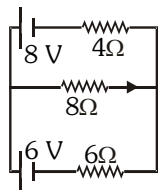10. The current in  $8\ \Omega$  resistance is (as per given circuit)



- (1) 0.69 A (2) 0.92 A  
(3) 1.30 A (4) 1.6 A

**CE0197**

11.  $n$  identical cells, each of emf  $E$  and internal resistance  $r$ , are joined in series to form a closed circuit. One of the cell  $A$  is joined with reversed polarity. The potential difference across each cell except  $A$ , is :-

- (1)  $\frac{2\varepsilon}{n}$  (2)  $\frac{n-1}{n}\varepsilon$   
(3)  $\frac{n-2}{n}\varepsilon$  (4)  $\frac{2n}{n-2}\varepsilon$

**CE0199**

12. In the above question, the potential difference across  $A$  is :-

- (1)  $\frac{2\varepsilon}{n}$  (2)  $\varepsilon\left(1 - \frac{1}{n}\right)$   
(3)  $2\varepsilon\left(1 - \frac{1}{n}\right)$  (4)  $\varepsilon\left(\frac{n-2}{n}\right)$


**CE0200**

13. A heater takes 40 minutes to boil a given amount of water. Its coil is cut and  $\frac{1}{4}$ th of its length is used in the heater now. How much time will it take now to boil the same amount of water using the same source ?

- (1) 10 minutes (2) 12 minutes  
(3) 15 minutes (4) 8 minutes

**CE0201**

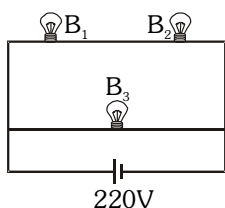14. A 100 W bulb  $B_1$  and two 60 W bulbs  $B_2$  and  $B_3$ , are connected to a 220 V source, as shown in Figure. Now  $P_1$ ,  $P_2$  and  $P_3$  are the output powers of the bulbs  $B_1$ ,  $B_2$  and  $B_3$  respectively. Then:




- (1)  $P_1 > P_2 = P_3$  (2)  $P_1 > P_2 > P_3$   
(3)  $P_1 < P_2 = P_3$  (4)  $P_1 < P_2 < P_3$

**CE0202**


15. A student connects a voltmeter, ammeter and resistance according to the circuit given. If the voltmeter reading is 20 V and ammeter reading is 4 A, then the resistance will be

- (1) equal to 5  $\Omega$   
(2) more than 5  $\Omega$   
(3) less than 5  $\Omega$   
(4) less or more depending on the material of wire

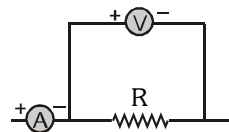

**CE0204**

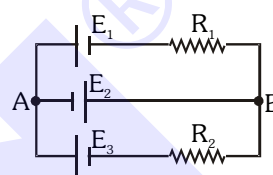16. In the circuit shown here,  $E_1 = E_2 = E_3 = 2\text{ V}$  and  $R_1 = R_2 = 4\text{ ohms}$ . The current flowing between points  $A$  and  $B$  through battery  $E_2$  is :



- (1) zero  
(2) 2 A from A to B  
(3) 2 A from B to A  
(4) none of the above

**CE0205**

17. If specific resistance of a potentiometer wire is  $10^{-7}\ \Omega\text{ m}$  and current flow through it is 0.1 A, cross-sectional area of wire is  $10^{-6}\text{ m}^2$  then potential gradient will be :-

- (1)  $10^{-2}\text{ volt/m}$  (2)  $10^{-4}\text{ volt/m}$   
(3)  $10^{-6}\text{ volt/m}$  (4)  $10^{-8}\text{ volt/m}$

**CE0207**

18. For a cell, the terminal potential difference is 2.2 V when circuit is open which reduces to 1.8 V when it is connected to a resistance of  $R = 5\ \Omega$ ; then internal resistance of the cell is :-

- (1)  $\frac{10}{9}\ \Omega$  (2)  $\frac{9}{10}\ \Omega$   
(3)  $\frac{11}{9}\ \Omega$  (4)  $\frac{5}{9}\ \Omega$


**CE0208**

19.  $n$  identical cells whether joined together in series or in parallel, give the same current, when connected to an external resistance ' $R$ '. The internal resistance of each cell is :-

- (1)  $r = nR$  (2)  $r = R$   
(3)  $r = \frac{R}{n}$  (4)  $r = n^2R$

**CE0209**

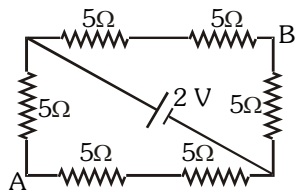
20. The potential difference between the points A and B in the following circuit shown in the figure is :-



- (1)  $\frac{2}{3}$  volts (2)  $\frac{4}{5}$  volts  
(3)  $\frac{8}{9}$  volts (4) 2 volts

CE0210

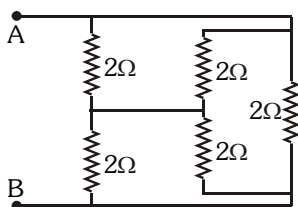21. The equivalent resistance across AB is :-



- (1) 1 Ω (2) 2 Ω (3) 3 Ω (4) 4 Ω


CE0211

22. When a voltmeter and an ammeter are connected one by one across the terminals of a cell respectively measures 5 V and 10 A. Now all meters are removed and only a resistance of 2 Ω is connected across the terminals of the cell. The current flowing through this resistance is :-

- (1) 7.5 A (2) 5.0 A  
(3) 2.5 A (4) 2.0 A

CE0212

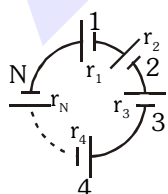23. A group of N cells each of whose emf varies directly with the internal resistance as per the equation  $E_N = 1.5 r_N$  are connected as shown in the figure. The current in the circuit is :-



- (1) 5.1 A (2) 0.51 A  
(3) 1.5 A (4) 0.15 A

CE0213

24. The length of a wire of a potentiometer is 100 cm and the emf of its standard cell is E volts. It is employed to measure the e.m.f. of a battery whose internal resistance is 0.5 Ω. If the balance point is obtained at  $\ell = 30$  cm from the positive end, the e.m.f. of the battery is :-

- (1)  $\frac{30E}{100}$  (2)  $\frac{30E}{100.5}$   
(3)  $\frac{30E}{(100 - 0.5)}$  (4)  $\frac{30(E - 0.5)}{100}$

CE0214

25. Two wires of resistance  $R_1$  and  $R_2$  at  $0^\circ \text{C}$  have temperature coefficients of resistance  $\alpha_1$  and  $\alpha_2$  respectively. These are joined in series. The effective temperature coefficient of resistance is :-

- (1)  $\frac{\alpha_1 + \alpha_2}{2}$  (2)  $\sqrt{\alpha_1 \alpha_2}$   
(3)  $\frac{\alpha_1 R_1 + \alpha_2 R_2}{R_1 + R_2}$  (4)  $\frac{\sqrt{R_1 R_2 \alpha_1 \alpha_2}}{\sqrt{R_1^2 + R_2^2}}$

CE0215

26. A battery is charged at a potential of 15 V for 8 hours when the current flowing is 10 A. The battery on discharge supplies a current of 5 A for 15 hours. The mean terminal voltage during the discharge is 14 V. The "Watt hour" efficiency of the battery is :

- (1) 80% (2) 90% (3) 87.5% (4) 82.5%


CE0216

**27.** A galvanometer of 50 ohms resistance has 25 divisions. A current of  $4 \times 10^{-4}$  amperes gives a deflection of one division. To convert this galvanometer into a voltmeter having a range of 25 volts, it should be connected with a resistance of :-

- (1) 2450  $\Omega$  in parallel      (2) 2550  $\Omega$  in series  
(3) 2450  $\Omega$  in series      (4) 2500  $\Omega$  in parallel

**CE0217**

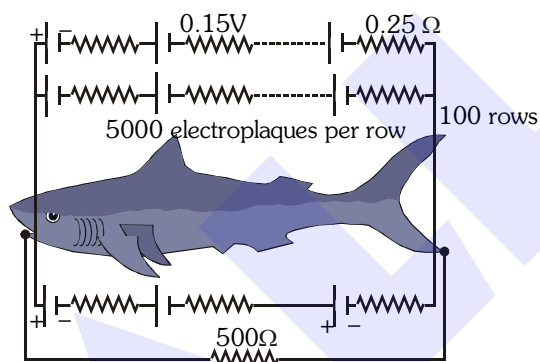
**28.** Eels are able to generate current with biological cells called electroplaques. The electroplaques in an eel are arranged in 100 rows, each row stretching horizontally along the body of the fish containing 5000 electroplaques. The arrangement is suggestively shown below. Each electroplaques has an emf of 0.15 V and internal resistance of 0.25  $\Omega$ . The water surrounding the eel completes a circuit between its head and its tail. If the water surrounding it has a resistance of 500  $\Omega$ , the current an eel can produce in water is about :-



- (1) 1.5 A      (2) 3.0 A      (3) 15 A      (4) 30 A

**CE0218**

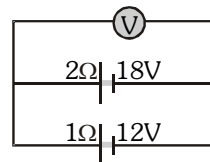**29.** Two batteries, one of emf 18 volts and internal resistance 2  $\Omega$  and the other of emf 12 volts and internal resistance 1  $\Omega$ , are connected as shown. The voltmeter V will record a reading of :-



- (1) 18 volts      (2) 30 volts  
(3) 14 volts      (4) 15 volts

**CE0219**

### EXERCISE-III (Analytical Questions)

### ANSWER KEY

Que.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
Ans.	3	3	1	3	1	1	3	1	3	1	1	3	1	4	2
Que.	16	17	18	19	20	21	22	23	24	25	26	27	28	29	
Ans.	2	1	1	2	1	1	4	3	1	3	3	3	1	3	