

Enthusiast Course COURSE

PHASE : Speed & Accuracy Test

TARGET : PRE-MEDICAL 2023

Test Type : PRACTICE TEST

Test Pattern : NEET (UG)

TEST DATE : _____

ANSWER KEY

Q.	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
A.	3	1	3	3	3	1	4	2	3	4	3	4	3	1	3	3	3	2	2	2	2	1	3	4	3	2	1	3	4	1
Q.	31	32	33	34	35	36	37	38	39	40	41	42	43	44	45															
A.	2	1	3	3	2	2	3	3	2	1	2	1	3	2	2															

HINT - SHEET



Click Here To Join our Telegram Channel

1. Ans (3)

$V_{in} = 10V$; KVL in i/p loop

$V_{BE} = 0V$ $V_{in} = I_B R_b + V_{BE}$

$V_{CE} = 0$ $V_{in} = I_B R_b + V_{BE}$

$I_B = \frac{10}{400} \times 10^{-3} = 0.025mA$

KVL in o/p loop

$V_{CC} = I_C R_C + V_{CE}$

$\Rightarrow 10 = I_C \times 3 \times 10^3$

$I_C = 10/3 \times 10^3 = 3.33mA$


2. Ans (1)

for -ve half cycle diode is RB hence o/p across resistance is zero (0V)

+ve half cycle diode is FB hence o/p across resistance is +1V

3. Ans (3)

$V_{in} > V_z$ hence diode is at B/D

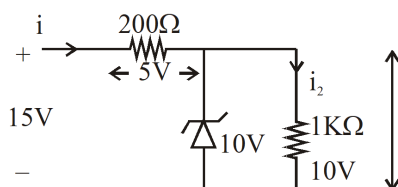

$i = 5/200 = 0.025A = 25mA$

$I_L = 10/10^3 = 10mA$

$i_Z = i - I_L = 25 - 10 = 15mA$

5.

Ans (3)

$n_i^2 = n_e \times n_h$

$$\Rightarrow n_e = \frac{n_i^2}{n_h} = \frac{(0.6 \times 10^{12})^2}{4 \times 10^{20}}$$

$$= \frac{0.36 \times 10^{24}}{4 \times 10^{20}} = 0.09 \times 10^4$$

$$= 9 \times 10^2 m^{-3}$$

6.

Ans (1)

current gain (β) =

$$\frac{\Delta I_C}{\Delta I_B} = \frac{(15 - 10) \times 10^{-3}}{(150 - 50) \times 10^{-6}}$$


$$= \frac{5 \times 10^{-3}}{100 \times 10^{-6}} = \frac{5000}{100} = 50$$

7.

Ans (4)

In reverse bias -ve terminal to P side & +ve terminal to N side, with increase in R.B potential width of depletion layer increase.

10. Ans (4)

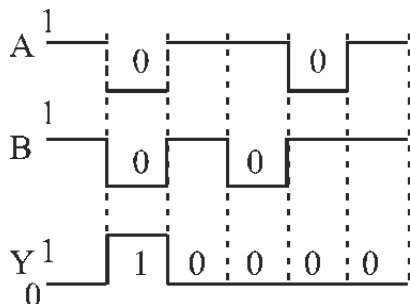

A	B	Y
1	1	0
0	0	1
1	1	0
1	0	0
0	1	0

11. Ans (3)

$$A_v = \beta \frac{R_L}{R_i} \left\{ \because \beta = A_v \frac{R_i}{R_L} \right\}$$


$$A_p = \beta A_v$$

$$A_p = A_v^2 \frac{R_i}{R_L} = (25)^2 \times \frac{50}{250} = \frac{625}{5} = 125$$

12. Ans (4)

Transistor is used as an inverter or switch b/w (I) & (III) region of V.I curve.

13. Ans (3)

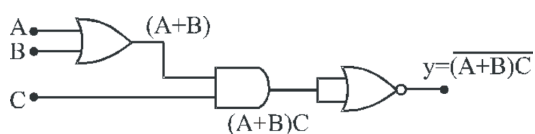

put A = 0 B = 1 C = 0

$$y = 1$$

put A = 0 ; B = 0 ; C = 1

$$y = 1$$

14. Ans (1)

$$\frac{hc}{\lambda} \geq E_g$$

$$\Rightarrow \lambda \frac{hc}{E_g} = \frac{12400}{1.8} = 6,888 \text{ \AA}$$

15. Ans (3)


$$\Delta I_B = (200 - 150) \times 10^{-6} = 50 \times 10^{-6} \text{ A}$$

$$\Delta I_C = (15 - 10) \times 10^{-3} = 5 \times 10^{-3} \text{ A}$$

$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{5 \times 10^{-3}}{50 \times 10^{-6}} = \frac{5 \times 10^3}{50} = \frac{5000}{50} = 100$$

$$A_v = \beta \frac{R_C}{R_B} = 100 \times \frac{20 \times 10^3}{1 \times 10^3} = 2000$$

16. Ans (3)

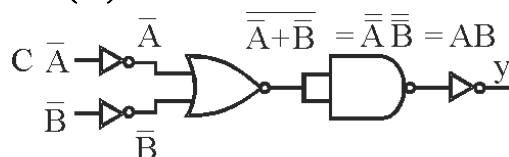

$$y = \overline{\overline{A} \cdot \overline{B}}$$

$$y = A \cdot B$$

AND Gate

17. Ans (3)

$$h\nu = 2.6 \text{ eV ;}$$

$$\nu = \frac{2.6 \times 1.6 \times 10^{-19}}{6.6 \times 10^{-34}}$$

$$= 0.630 \times 10^{15}$$

$$= 6.3 \times 10^{14} \text{ Hz}$$

18. Ans (2)

$$V_0 = A \left(V_i + \frac{10}{100} V_0 \right) \{ \because V_0 = 50 V_i \}$$

$$50 V_i = A \left(V_i + \frac{50}{10} V_0 \right)$$

$$50 V_i = A 6 V_i$$


$$A = \frac{50}{6} = 8.33$$

19. Ans (2)

$$\text{Power gain } A_p = \beta A_v = A_v^2 \frac{R_i}{R_L}$$

$$P_v = (100)^2 \times \frac{50}{200} = \frac{100 \times 100}{4} = 2500$$

20. Ans (2)

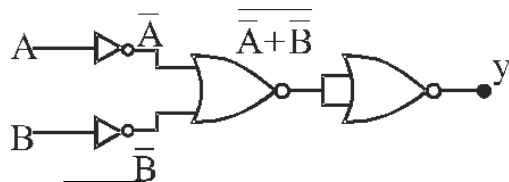

$$y = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} + \overline{B}} = A \cdot B$$

NAND gate

21.

Ans (2)

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$= \frac{(12-8) \times 10^{-3}}{(300-250) \times 10^{-6}}$$

$$= \frac{4 \times 10^{-3}}{50 \times 10^{-6}}$$

$$= \frac{4}{50} \times 10^3$$

$$= \frac{4000}{50} = 80$$

22. Ans (1)

The kinetic energy of the most energetic electrons is

$$K = \frac{hc}{\lambda} - \phi$$

$$= \frac{1242 \text{ eV nm}}{450 \text{ nm}} - 2.0 \text{ eV}$$

$$= 0.76 \text{ eV} = 1.2 \times 10^{-19} \text{ J}$$

The linear momentum = mv

$$= \sqrt{2mK}$$

$$= \sqrt{2 \times (9.1 \times 10^{-31} \text{ kg}) \times (1.2 \times 10^{-19} \text{ J})}$$

$$= 4.67 \times 10^{-25} \text{ kgms}^{-1}$$

When a charged particle is sent perpendicular to a magnetic field, it goes along a circle of radius

$$r = \frac{mv}{qB}$$


$$\text{Thus, } 0.20 \text{ m} = \frac{4.67 \times 10^{-25} \text{ kg ms}^{-1}}{(1.6 \times 10^{-19} \text{ C}) \times B}$$

$$\text{or, } B = \frac{4.67 \times 10^{-25} \text{ kg ms}^{-1}}{(1.6 \times 10^{-19} \text{ C}) \times (0.20 \text{ m})}$$

$$= 1.46 \times 10^{-5} \text{ T}$$

23. Ans (3)

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

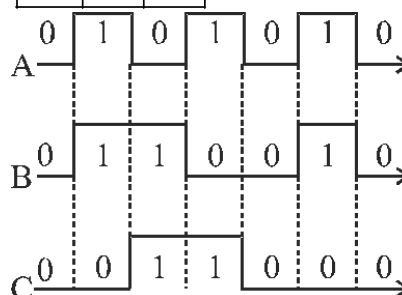

X-OR Gate

24. Ans (4)

Semiconductors have negative temp. coefficient

temp $\uparrow$ $\rho \downarrow$ $\sigma \uparrow$

temp $\downarrow$ $\rho \uparrow$ $\sigma \downarrow$

25. Ans (3)

Solar cell is always unbiased

27. Ans (1)

$$V_{dc} = \frac{V_0}{\pi} = \frac{25}{\pi} \text{ (for H.W.R.)}$$

28. Ans (3)


NOR gate

X	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

29. Ans (4)

By increase RB potⁿ, effective barrier potential increases, thus width of depletion layer also increase.

30. Ans (1)

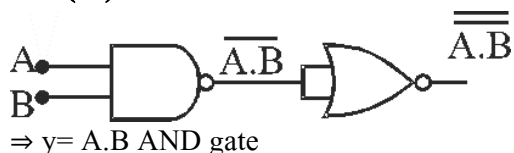

31. Ans (2)

In HWR ripple frequency is equal to source frequency.

32. Ans (1)

(depletion layer) depends only of type of biasing

36. Ans (2)

$$\text{HWR } V_{\text{rms}} = \frac{V_m}{2} = \frac{200}{2} = 100\text{V}$$

37. Ans (3)

Final P.D. across capacitor
 = peak value of the source voltage
 = $200\sqrt{2} = 283\text{ volt}$

38. Ans (3)

$$\begin{aligned}
 hv &= \frac{hc}{\lambda} \text{ J} = \frac{hc}{e\lambda} \text{ eV} \\
 &= \left(\frac{12400}{\lambda} \text{ eV} \right) = \frac{124}{248} \\
 &= 0.5 \text{ eV}
 \end{aligned}$$

42. Ans (1)

$$\begin{aligned}
 \beta &= \frac{\alpha}{1-\alpha} = \frac{0.96}{1-0.96} = 24 \\
 \therefore I_C &= \frac{V_C}{R} = \frac{0.5}{800} = 0.625\text{mA} \\
 I_B &= \frac{I_C}{\beta} \\
 &= \frac{0.625 \times 10^{-3}}{24} \\
 &= 26 \times 10^{-6} = 26\mu\text{A}
 \end{aligned}$$

44. Ans (2)

$$\begin{aligned}
 \alpha &= 0.98 \text{ and } \frac{R_{\text{out}}}{R_{\text{in}}} = 500 \\
 \therefore \beta &= \frac{\alpha}{1-\alpha} = \frac{0.98}{1-0.98} = 49
 \end{aligned}$$

Voltage gain

$$= \beta \frac{R_{\text{out}}}{R_{\text{in}}} = 49 \times 500 = 24500$$

Power gain

$$= \beta^2 \frac{R_{\text{out}}}{R_{\text{in}}} = (49)^2 500 = 1200500$$